



# *LINC transmitters: concepts, design and performance*

*A. L. Lacaita, S. Levantino and C. Samori*

Dipartimento di Elettronica e Informazione

Politecnico di Milano, Milano, Italy

*Feb. 19, 2009*




# Outline

Dipartimento  
Elettronica  
Informazione

- Motivation
- LINC Transmitter
  
- Impact of path imbalances
- Efficiency of Power combination
- Low-power Signal Separation
  
- Conclusions



# Wireless networks

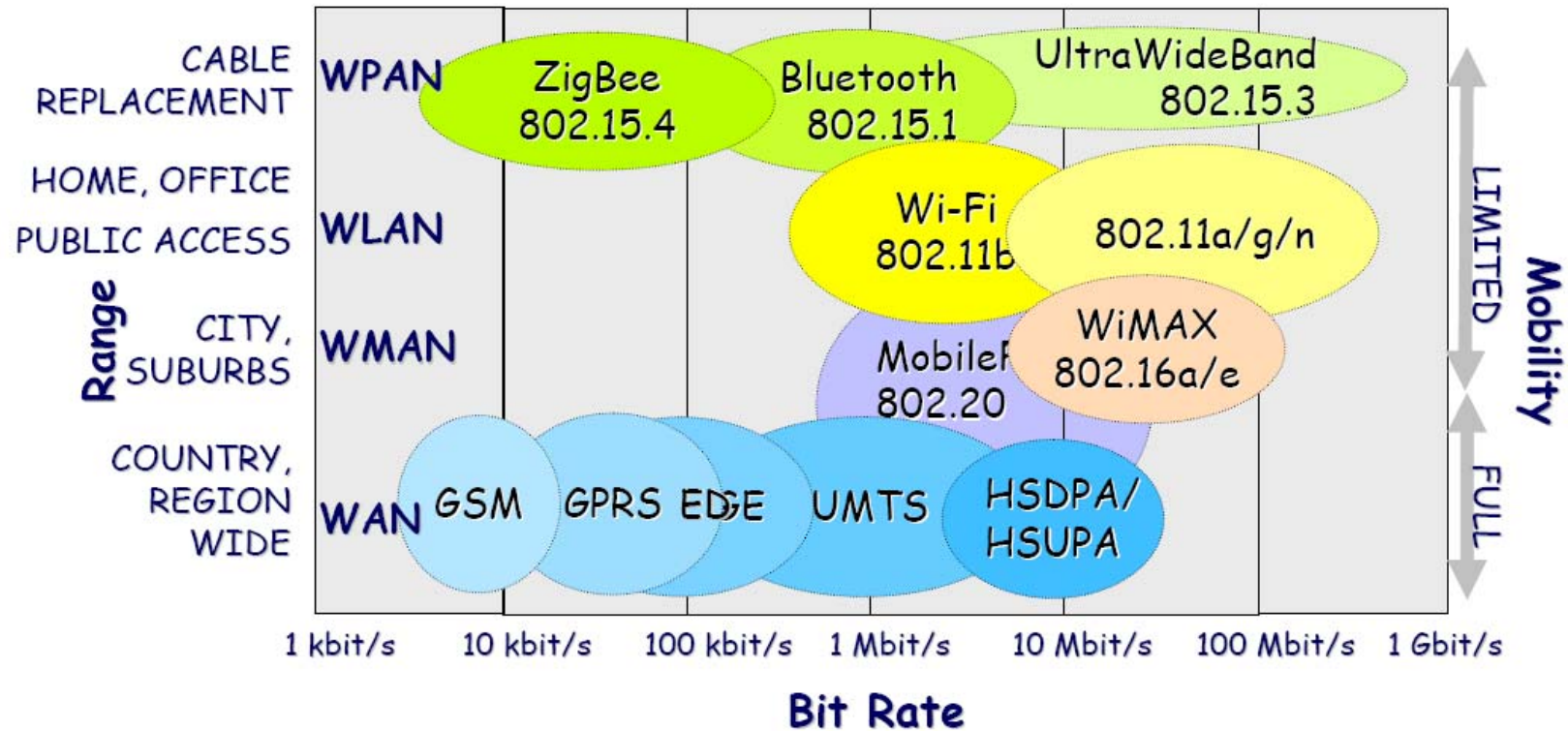



# TX Linearization techniques

Technique	Issues	Acceptance
Cartesian feedback	Symmetric feedback paths, feedback BW ~ signal BW, linear PA's, feedback demodulator	Popular
Polar-loop feedback	Asymmetric feedback paths, larger bandwidth, non-linear PA's	Medium
Envelope Elimination and Restoration	Asymmetric paths, BW wider than signal BW, AM/PM conversion	Low
LINC	2PA's, symmetric paths, BW wider than signal BW, recombination/separation efficiency	Under investigation




# Outline

Dipartimento  
Elettronica  
Informazione

- Motivation
- LINC Transmitter
- Impact of path imbalances
- Efficiency of Power combination
- Low-power Signal Separation
- Conclusions



# Basic Principle

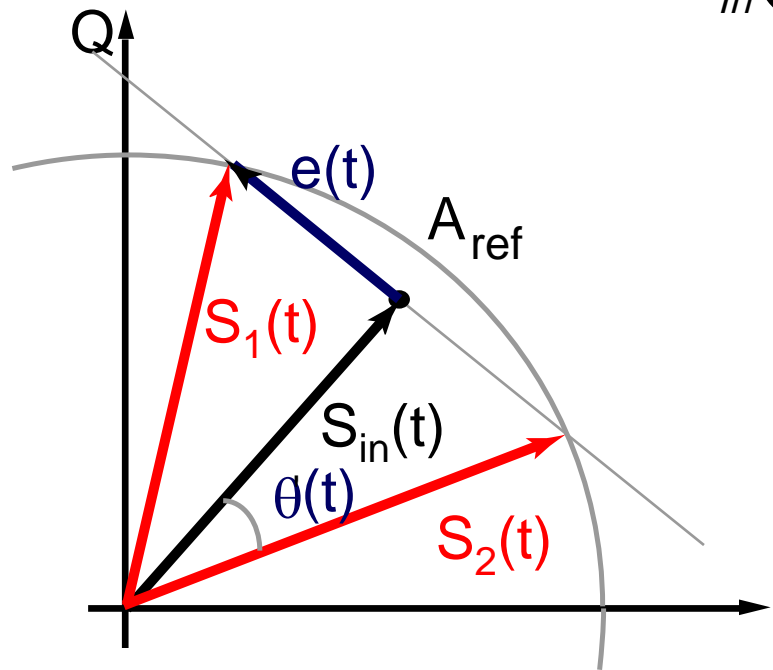

$$S_{in}(t) = A(t)e^{i\varphi(t)}$$

Separation

$$\begin{cases} S_1(t) = S_{in}(t) + e(t) \\ S_2(t) = S_{in}(t) - e(t) \end{cases}$$

---


---

$$\begin{aligned} S_{out}(t) &= G_{PA} \cdot [S_1(t) + S_2(t)] \\ &= 2G_{PA} \cdot S_{in}(t) \end{aligned}$$

**Amplification + Recombination**



## LINC TX

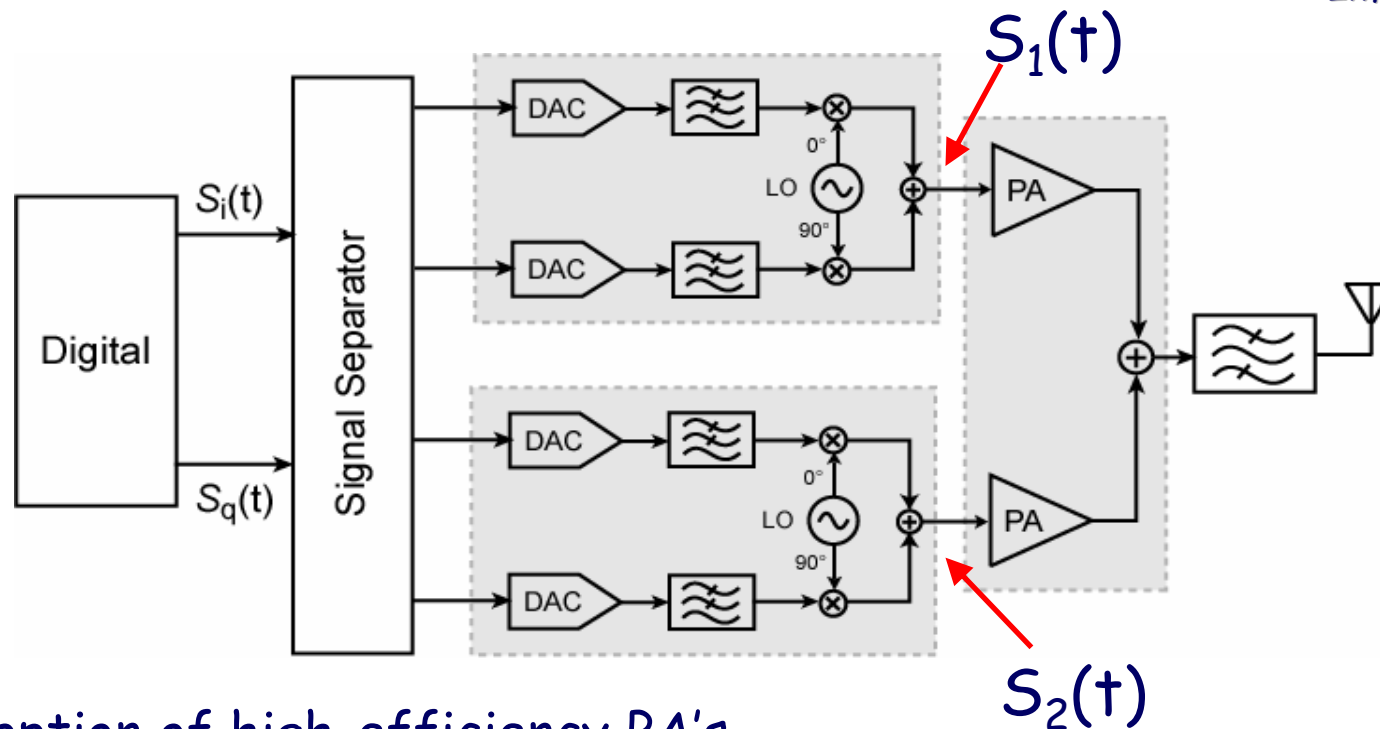

- Adoption of high-efficiency PA's
- Doubling the transceiver circuitry
- Major challenges:
  - ▶ accurate matching of the two amplification paths
  - ▶ efficient power recombination after PA's
  - ▶ low-power processing




# Outline

Dipartimento  
Elettronica  
Informazione

- Motivation
- LINC Transmitter
- **Impact of path imbalances**
- Efficiency of Power combination
- Low-power Signal Separation
- Conclusions



# Signal clipping of the separator

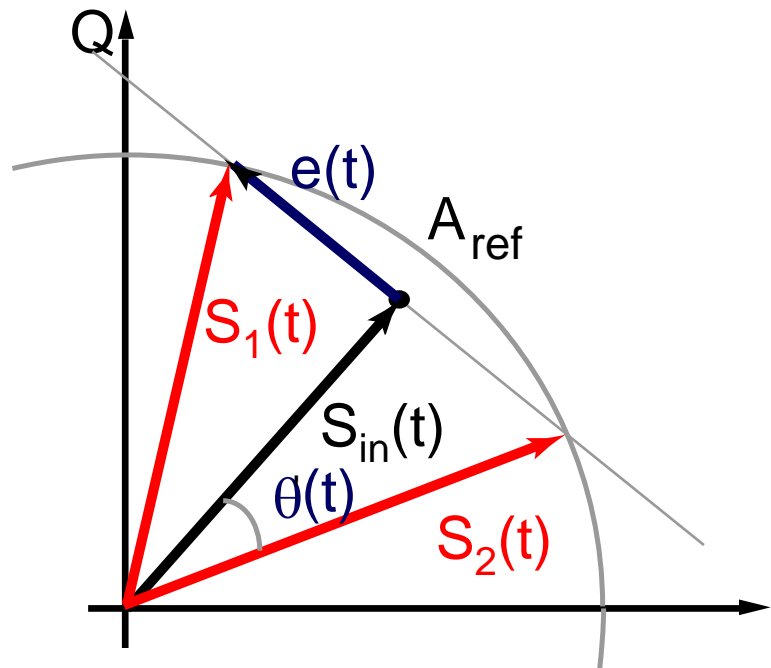

$\theta(t)$  is the outphasing angle



- If  $|S_{in}| > A_{ref}$ , the signal clips
- Margin from signal clipping

$$B = \sqrt{\frac{A_{ref}^2}{\langle S_{in}(t)^2 \rangle}}$$

- The larger the back-off, the larger  $|e(t)|$





# Gain and phase mismatches

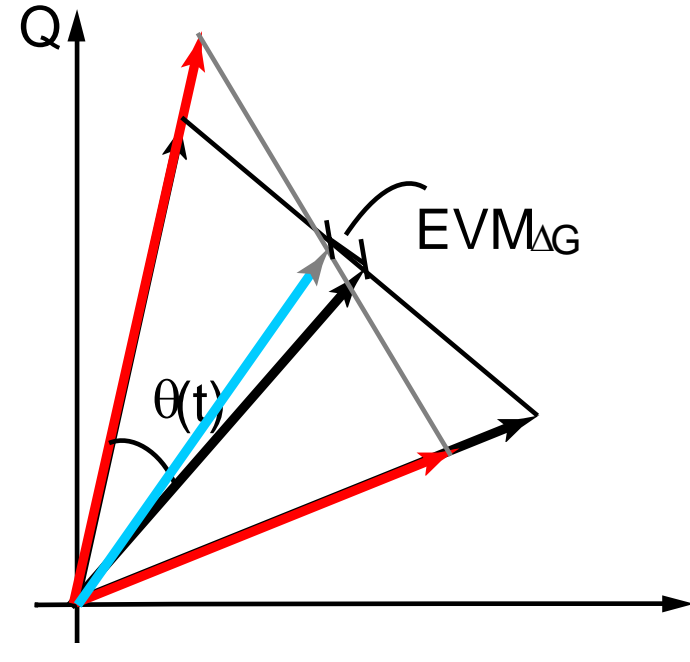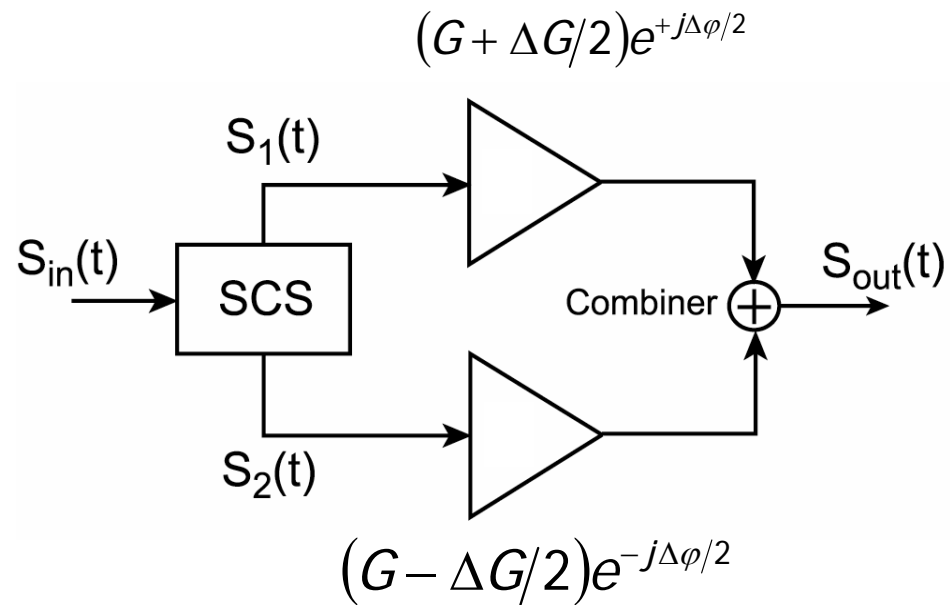

$$EVM = (B - 1) \cdot \left[ \left( \frac{\Delta\phi}{2} \right)^2 + \left( \frac{\Delta G}{2G} \right)^2 \right]$$



# Adjacent Channel Power Ratio

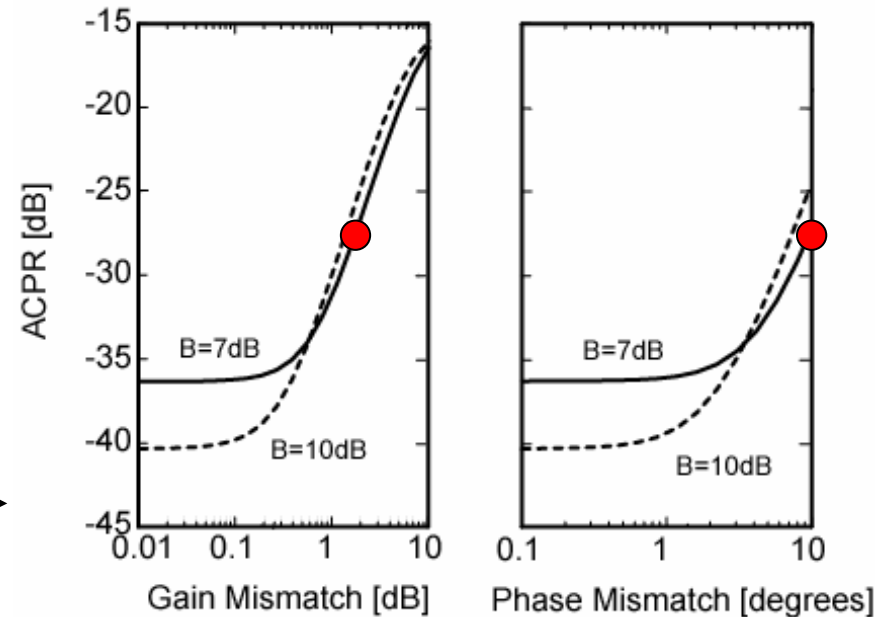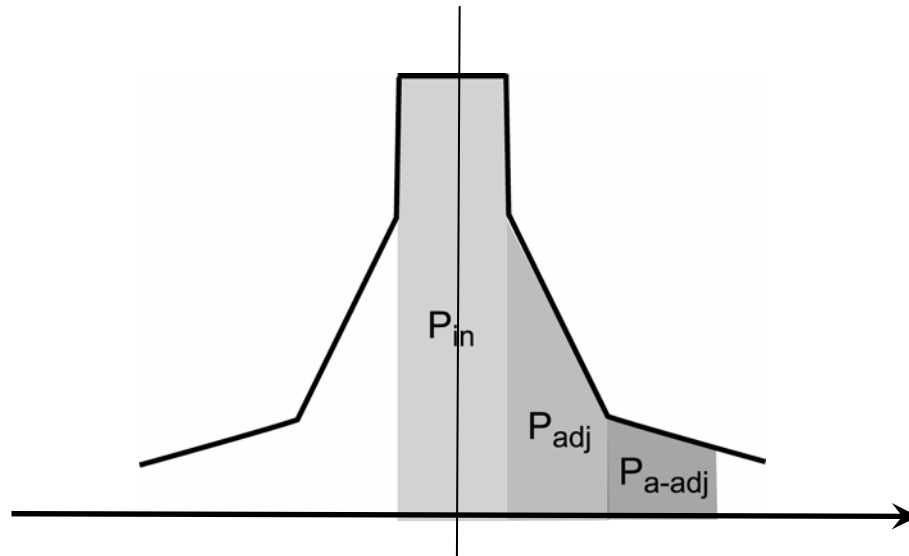

$$ACPR \propto (B-1) \cdot \left[ \left( \frac{\Delta\phi}{2} \right)^2 + \left( \frac{\Delta G}{2G} \right)^2 \right]$$

Back-off	Gain mismatch	Phase mismatch
7 dB	0.4 dB	2°

*L. Romanò et al, IEEE Trans. on Circuit and Systems-I, (2006)*



# Summary

- To avoid signal clipping a proper back-off of the signal separator should be set
- The larger the back-off the higher the sensitivity to path imbalances
- Mismatches of monolithic implementations can meet the requirements of high-bit rate wireless standards





# Outline

Dipartimento  
Elettronica  
Informazione

- Motivation
- LINC Transmitter
- Impact of path imbalances
- Efficiency of Power combination
- Low-power Signal Separation
- Conclusions



# Combiner efficiency

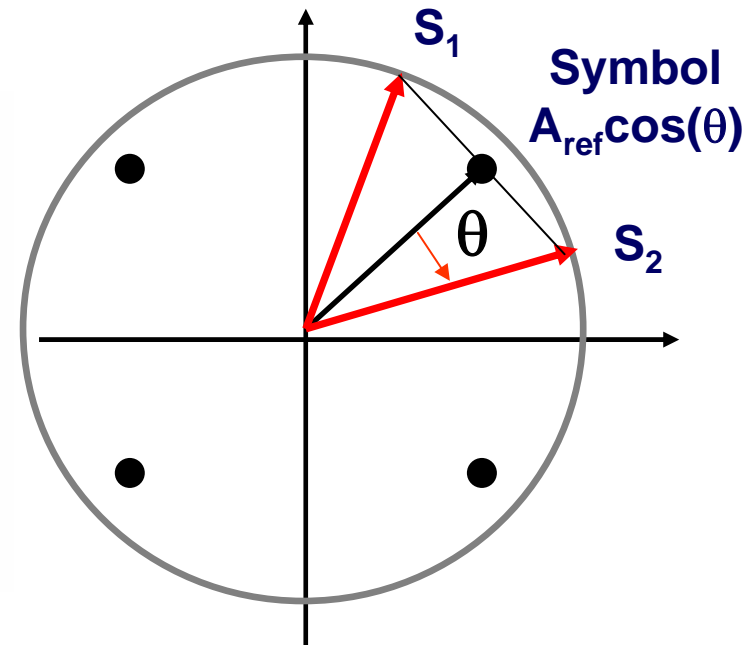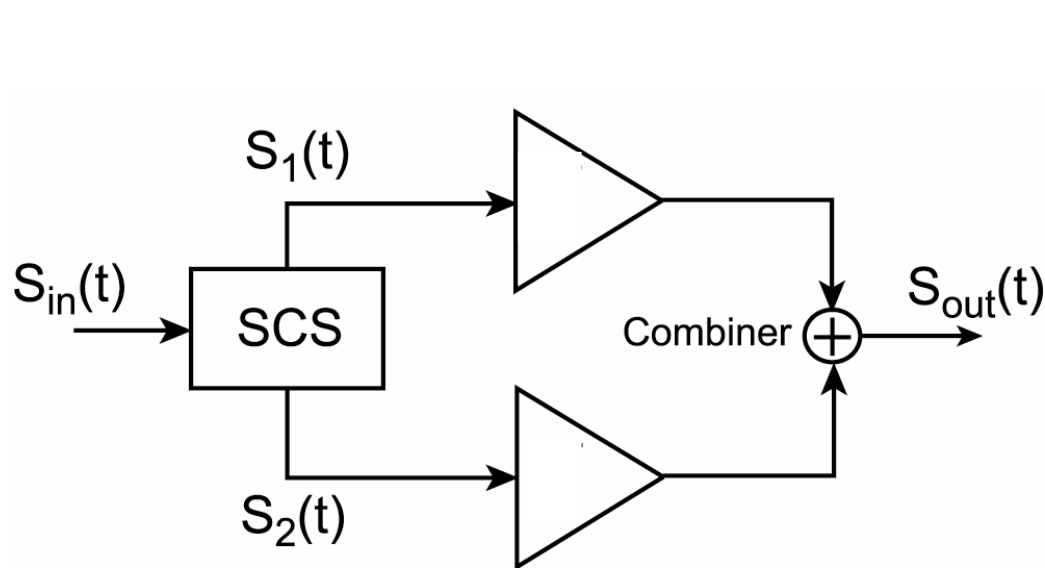


$\theta$  - outphasing angle

$$PAE \approx PAE^* \cdot \langle \cos^2(\theta) \rangle$$

- The higher  $\theta$ , the lower the PAE
- 20% max for IEEE 802.11 @7dB back-off




# Improving combiner efficiency

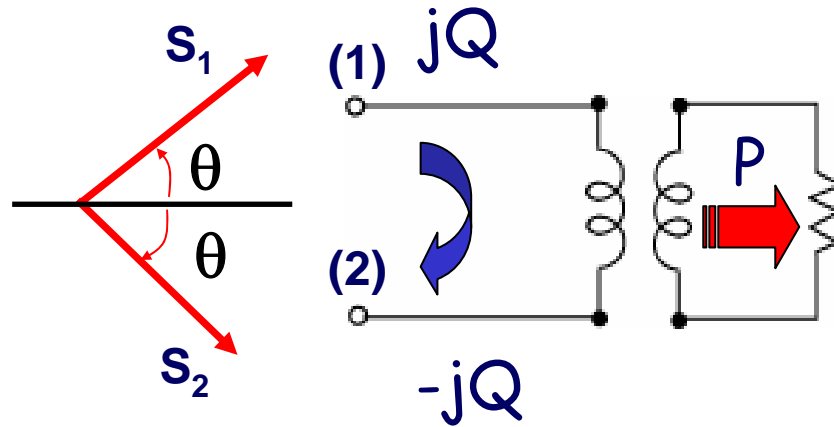



$$Z_{1-2} = R/2(1 \pm \cot \theta)$$

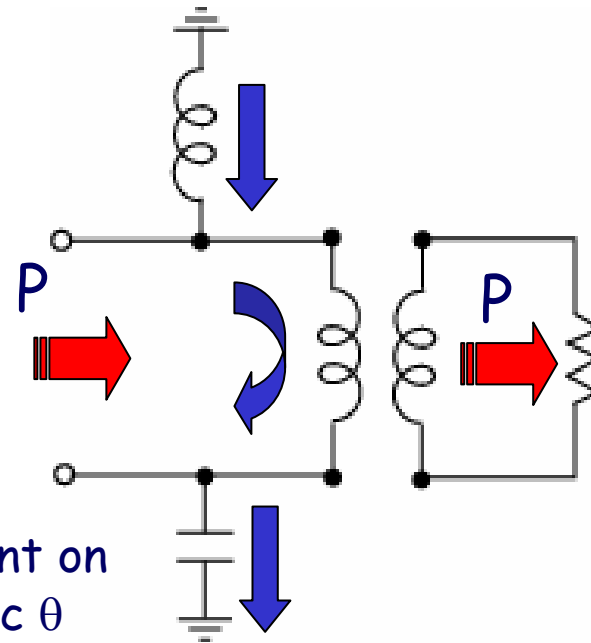- Chireix combiner
- Input impedance dependent on  $\theta$  - Tuning at some specific  $\theta$





# Performance

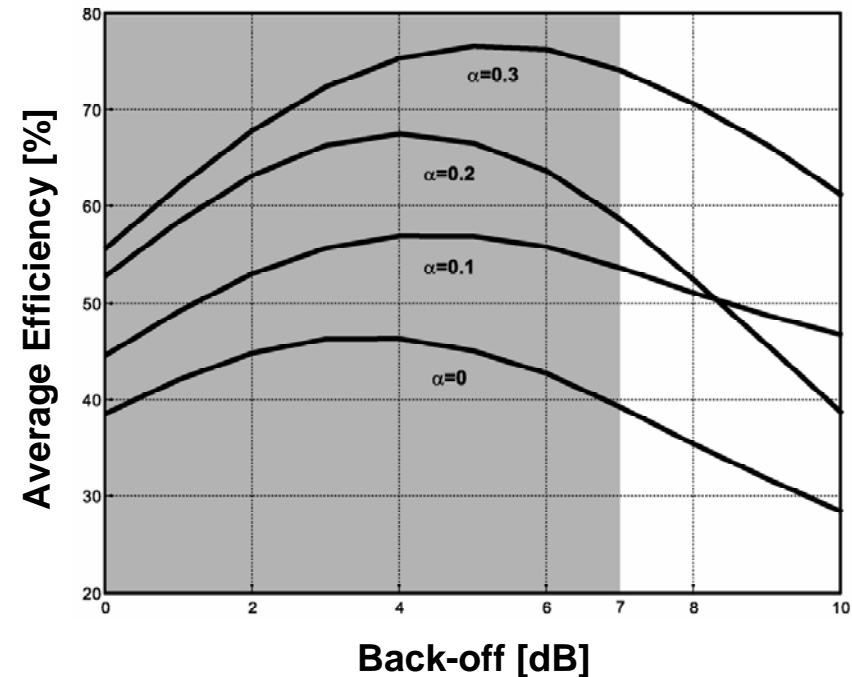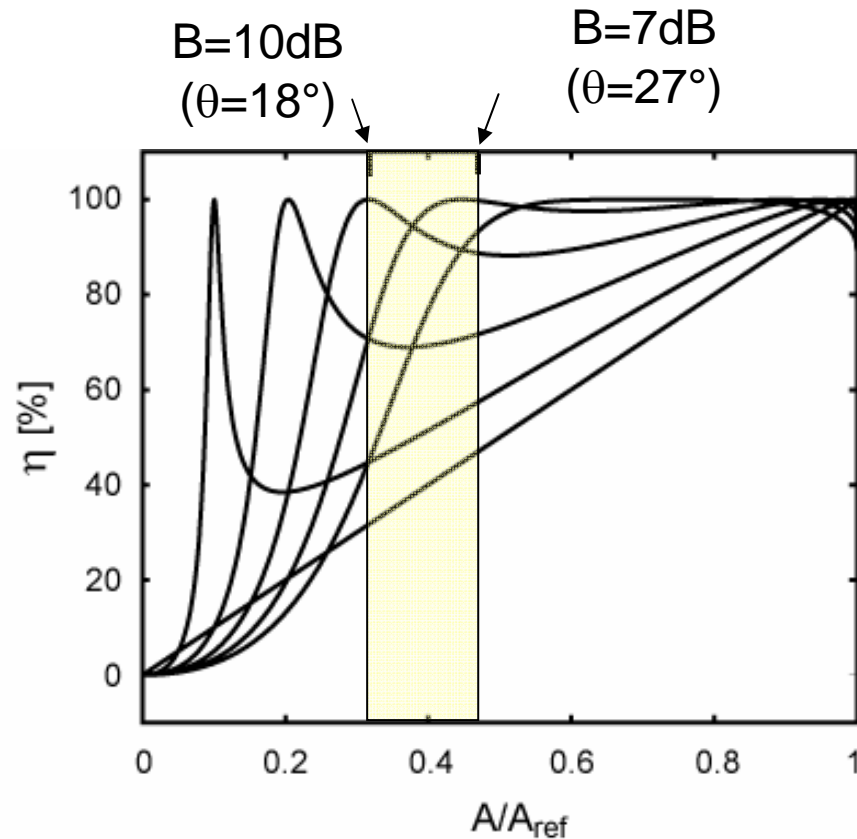

- IEEE 802.11g - Average efficiency larger than 70% @ 7dB back-off
- Reactance tuning - S. Moloudi et al. ISSCC'08



# Summary

- The efficiency of power combination is key figure for a LINC transmitter
- Loss-less recombination drains reactive power which degrades PA efficiency.
- Chireix recombination tunes out reactive components
- Reactance tuning may improve performance




# Outline

Dipartimento  
Elettronica  
Informazione

- Motivation
- LINC Transmitter
  
- Impact of path imbalances
- Efficiency of Power combination
- **Low-power Signal Separation**
  
- Conclusions




# LINC TX - Digital separation

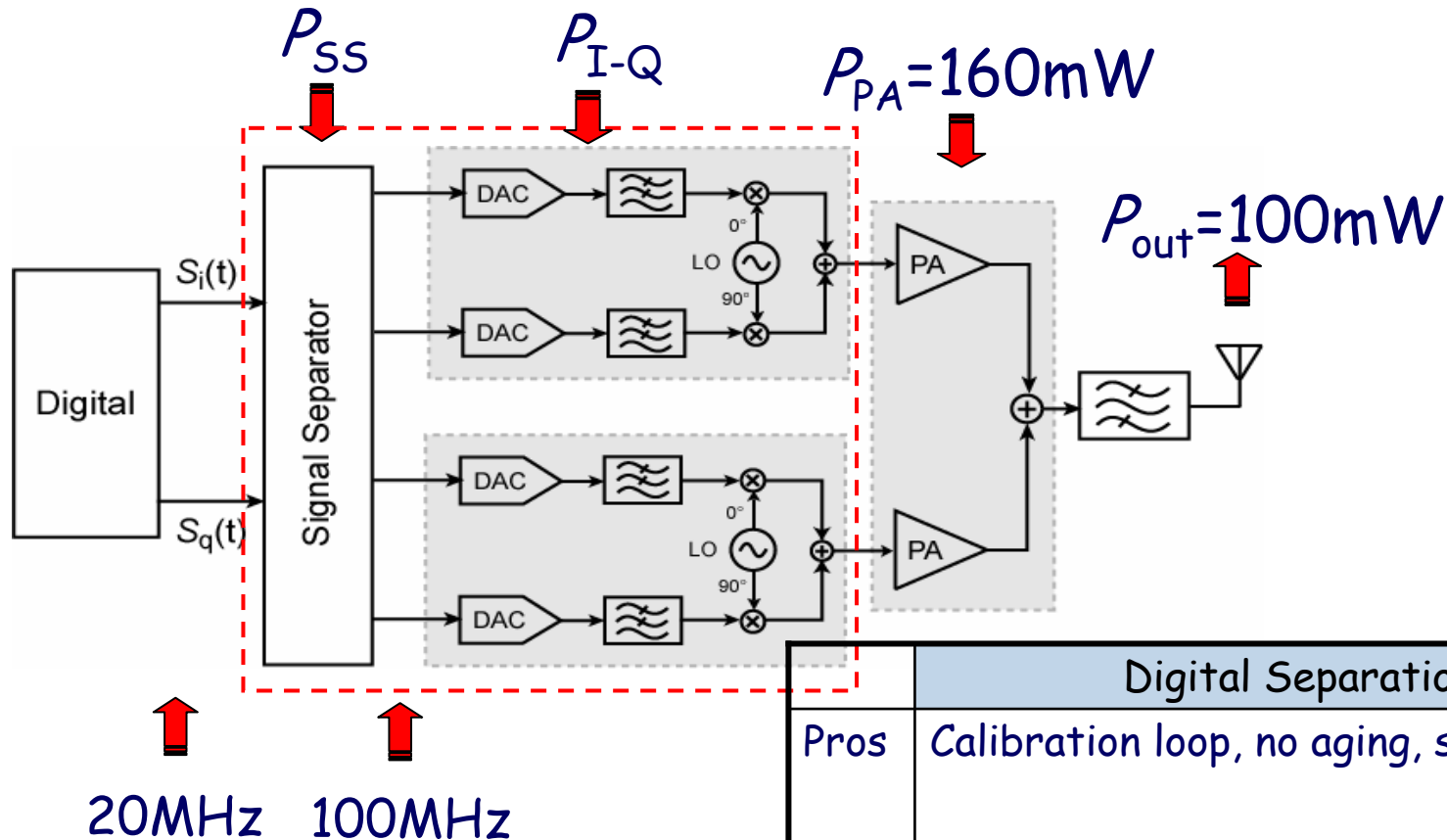

Digital Separation	
Pros	Calibration loop, no aging, scaling
Cons	Baseband BW = 5x Signal BW 4x DACs (10 bit)@400MHz 4x Filters (4th order)



# LINC TX: Digital vs. Analog Separation

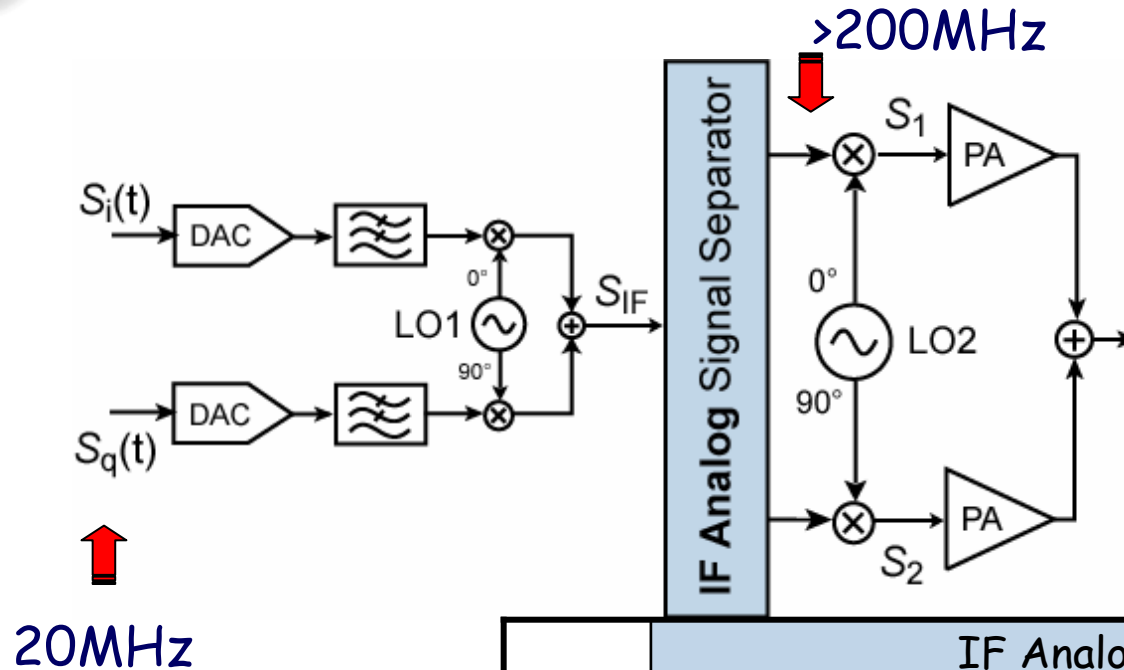


IF Analog Separation	
Pros	Baseband BW = Signal BW 2x DACs (10 bit) @ 40MHz 2x Filters (4th order)
Cons	Analog Separator BW = IF > Signal BW Requires complex filter and matching at IF Non-linear feedback

*B. Shi and L. Sundstrom, 2000 VLSI Symp. and 2001 CICC*



# LINC TX: Analog-BB SCS


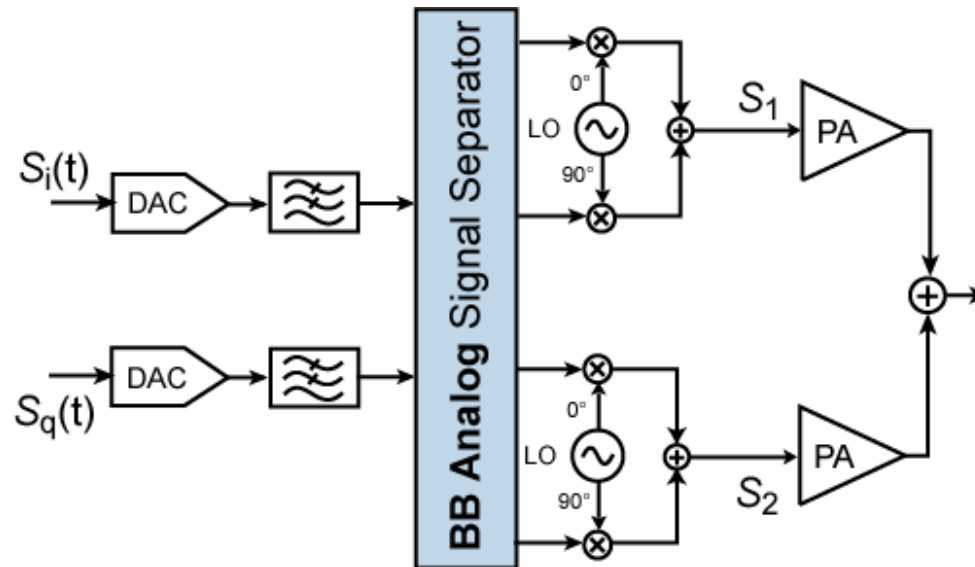


Baseband Analog Separation	
Pros	Baseband BW = Signal BW Analog Separator BW = Signal BW 2x DACs (10 bit) @ 40MHz 2x Filters (4th order)
Cons	Non-linear feedback

*L. Panseri et al., CICC 2006*  
*L. Romanò, C. Samori, A. Lacaita, Italian Patent*



# Analog-BB SCS: Implementation

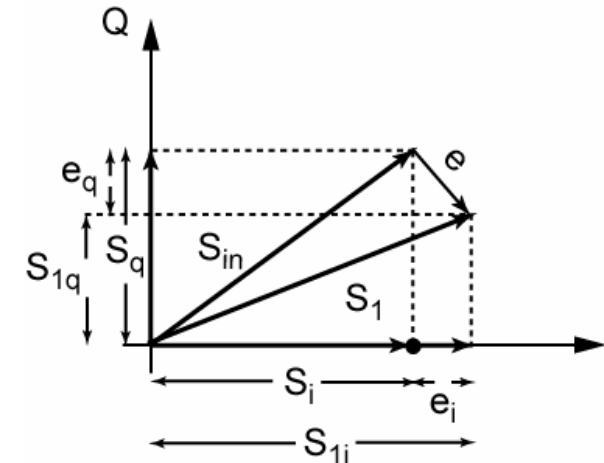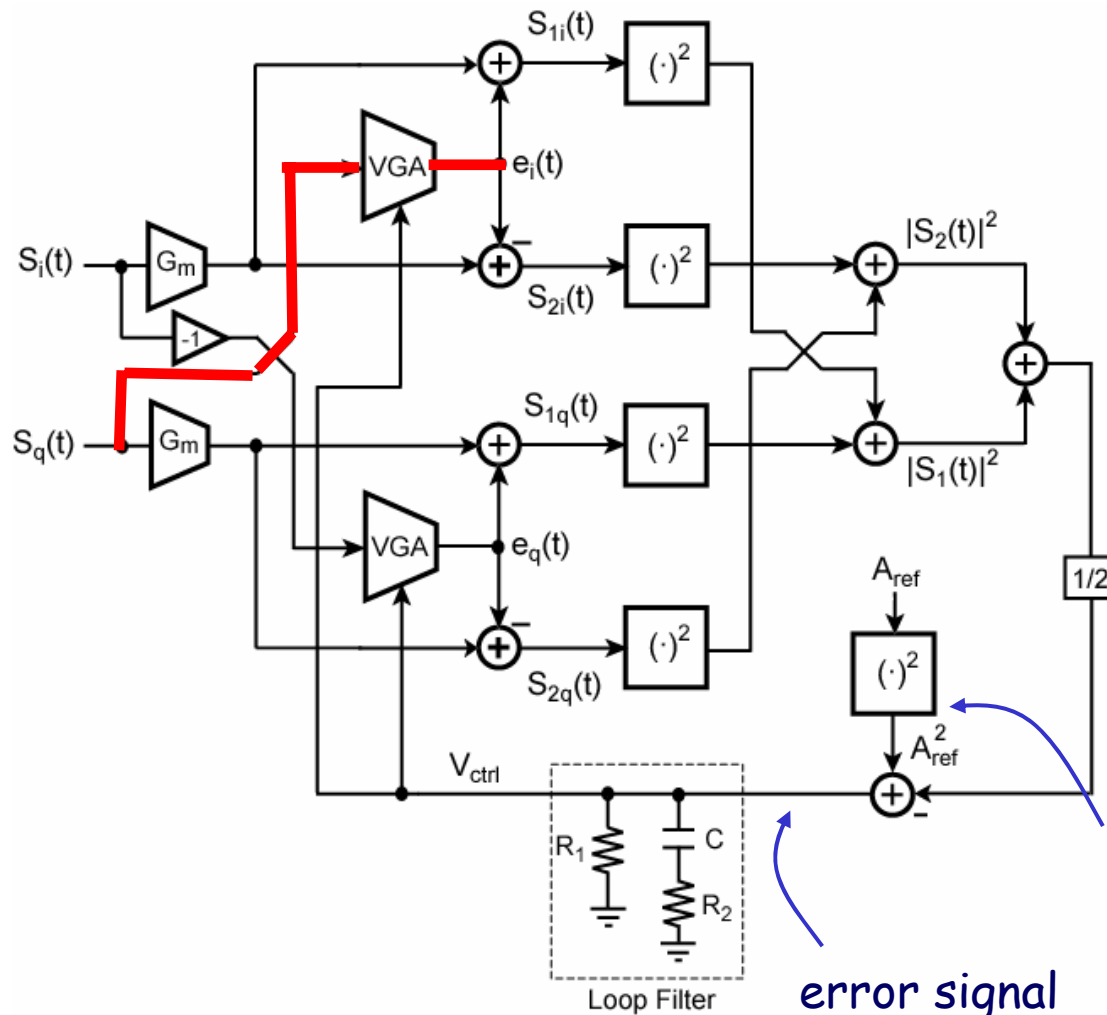

$$e(t) \sim -jS_{in} = -j[S_i + jS_q] = [S_q - jS_i]$$


error signal

The feedback forces  
 $(|S_1|^2 + |S_2|^2)/2 = A_{ref}^2$

L. Panseri et al., 2006 CICC  
L. Romanò, C. Samori, A. Lacaita, Italian Patent



# Non linear feedback


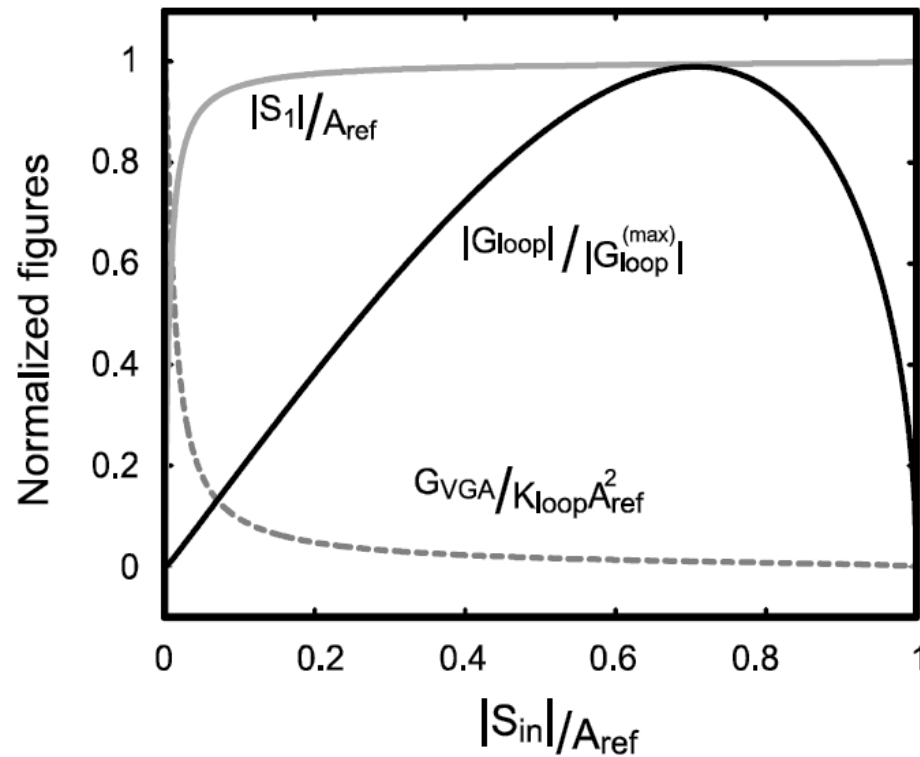


	Values
<i>Separator back-off</i>	7dB
<i>Maximum loop gain</i>	40dB
<i>VGA gain</i>	25dB -10dB
<i>Bandwidth</i>	200MHz


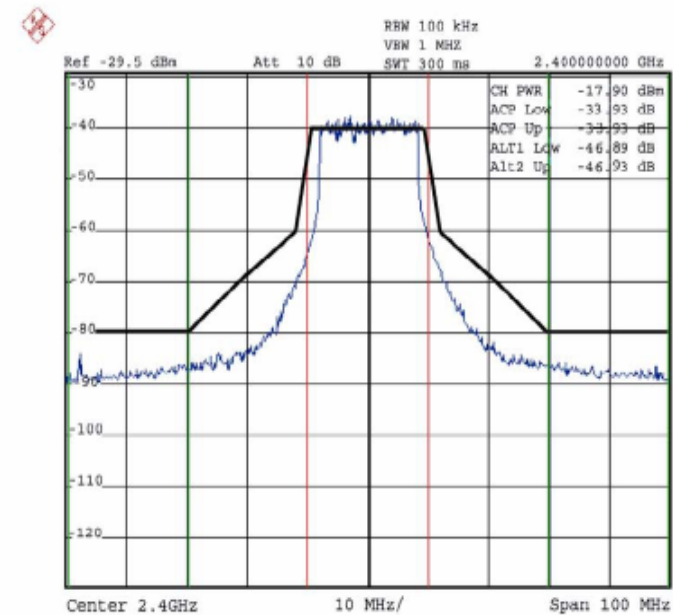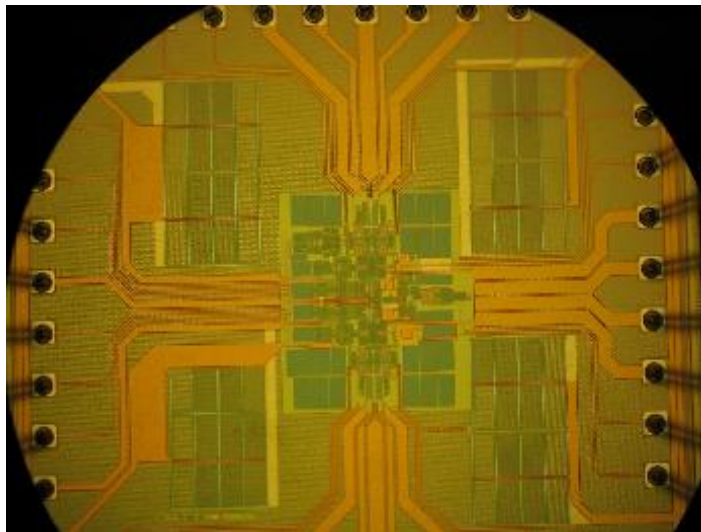
# Experimental measurements

Dipartimento  
Elettronica  
Informazione



- Technology: STM 0.25mm CMOS
- Core Area: 0.09 sq. mm
- Input signal BW: 16 MHz
- Dissipated Power: 45mW

*L. Panseri et al. JSSCC (2008)*

*This work has been supported by MEDEA+ A107 project*



# Conclusions

- Wireless high-data-rate communications are pushing towards high-efficiency and high-linearity TXs
- Among the linearization techniques, the LINC is a promising option, entailing no feedback and similar signal paths. Efficiency can be boosted up using switching PAs.
- In LINC, the signal separator back-off has to be chosen trading between linearity and sensitivity to paths imbalance. The required matching is obtainable in monolithic implementations.
- Signal recombination and separation are crucial for the TX efficiency:
  - ▶ Chireix recombination leads to satisfactory efficiency.
  - ▶ Analog signal separation avoids duplication of DACs and filters and leads to better efficiency.