



Design and Optimization of Passive UHF RFID Systems

Prof. Michel Declercq

Ecole Polytechnique Fédérale de Lausanne (EPFL)
Switzerland

OUTLINE

Introduction

Wireless Power Transmission

Communication Issues

Transponder (tag) and Reader Design

Conclusion

1 Introduction to RFID & Main issues


An exploding market
Principle
Near & Far-field
Ultra-High Frequency (UHF) Issues



1. INTRODUCTION





Principle

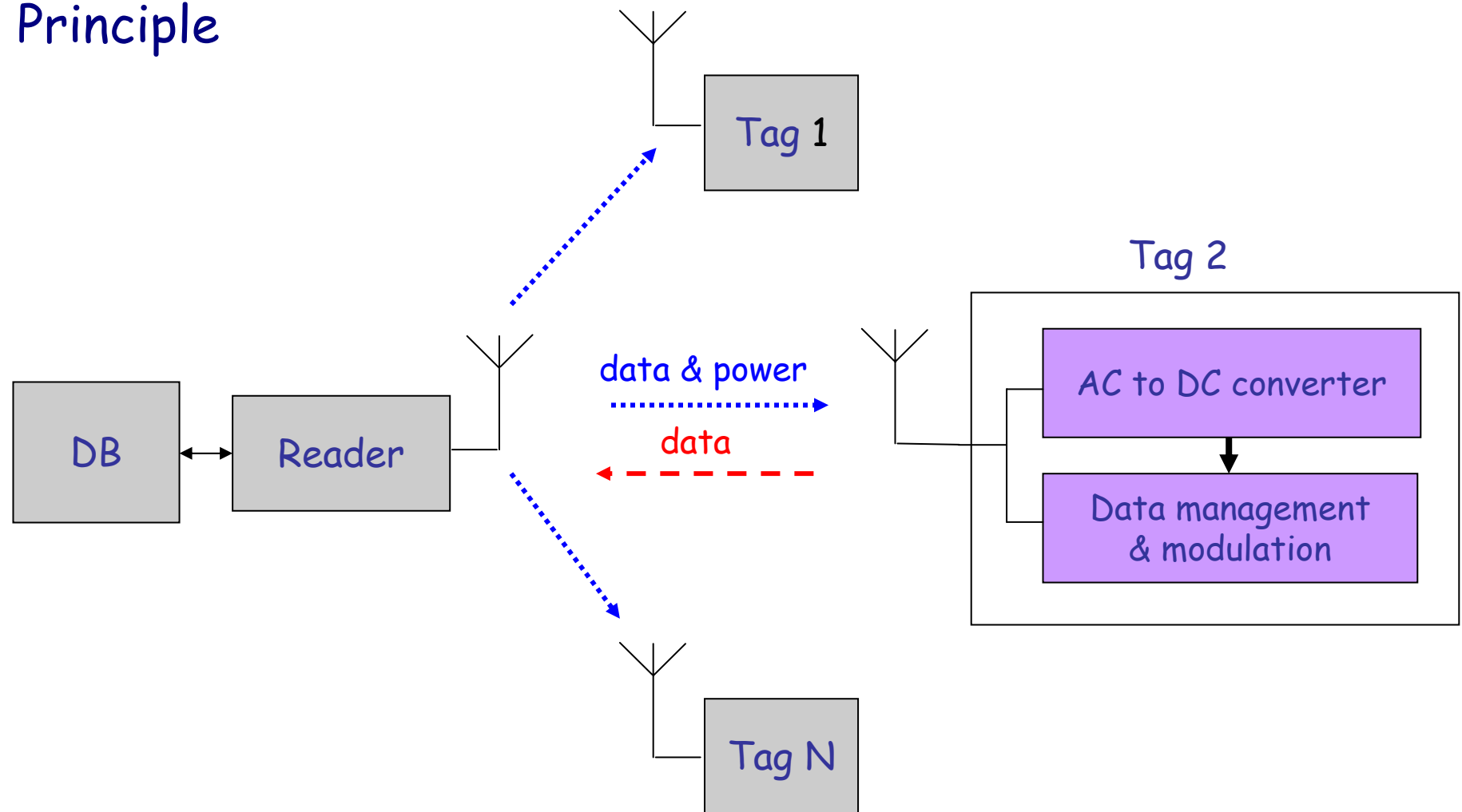

Near-field (low frequency applications, up to 100 MHz)

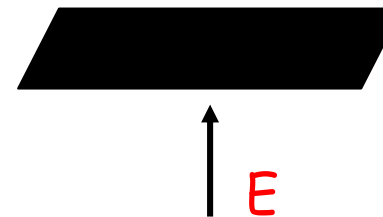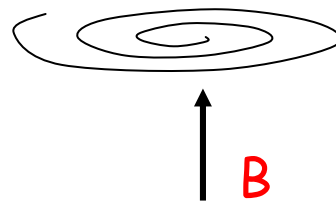- Starts in the direct neighborhood of any antenna up to $d = \frac{\lambda}{2\pi}$
- Usually inductive coupling (magnetic field)
- But can be capacitive coupling (electric field)
- Antennas have to be either coils for inductive coupling, or metallic surfaces for capacitive coupling
- Power decay in both cases is prop. to d^6



Far-field (high frequency applications, from 100 MHz)

- Far-field occurs at a distance of about $\frac{\lambda}{2\pi}$ from the antenna
- Electromagnetic coupling
- Antennas are typically of N-poles types (monopole, dipoles, etc.)
- Available Power varies with d^{-2} and λ^2 .


Wireless Power Transmission (WPT) in UHF passive systems

Some challenges:

- Power decay in the far-field is proportionnal to d^2
- Link budget is a function of d^{-4}
- RF to DC power conversion → Efficiency, Start-up voltage
- Tag and reader antenna design
- Type of Modulation for the backscattered signal
- Power management of tag circuits and signal encoding
- Reader design and sensitivity

Wireless Power Transmission (WPT) in UHF passive systems

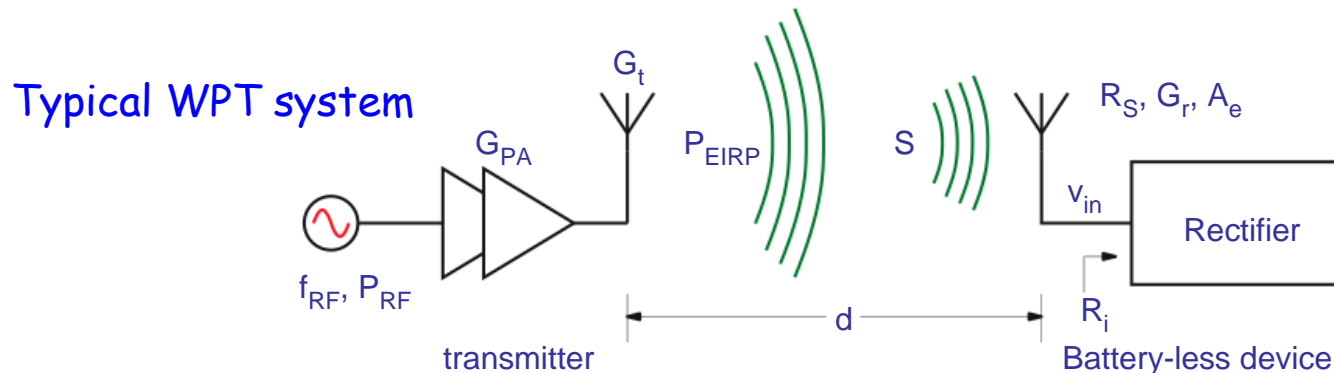A first estimation of power levels at tag (1/2):



- Power density at tag antenna: $S = P_{EIRP} \cdot \frac{1}{4\pi d^2}$
- Power collected by tag antenna and available to the load: $P_{AV} = A_E \cdot S$

With Antenna Aperture

$$A_E = \frac{\lambda^2}{4\pi} \cdot G_R$$

Wireless Power Transmission (WPT) in UHF passive systems

A first estimation of power levels at tag (2/2):

$$P_{AV} = S \cdot \frac{\lambda^2}{4\pi} \cdot G_R = P_{EIRP} \cdot G_R \cdot \frac{\lambda^2}{(4\pi d)^2} \quad F_{RiiS} \text{ Relation}$$

$$\lambda = 0,1224 \text{ m (2,45 Ghz)}$$

For $P_{EIRP} = 4 \text{ W}$

$G_R = 1 \text{ (0 dB): Antenna gain}$

d(m)	P_{AV} (W)
1 m	379 μ W
5 m	15.17 μ W
10 m	3.79 μ W
12 m	2.6 μ W

2 Wireless Power Transmission

Issue
Model
Results
Impacts on RFID Systems




2. Wireless Power Transmission


From low-voltage AC to high-voltage DC supply

Rectifier building blocks (1/2)

DC restorer

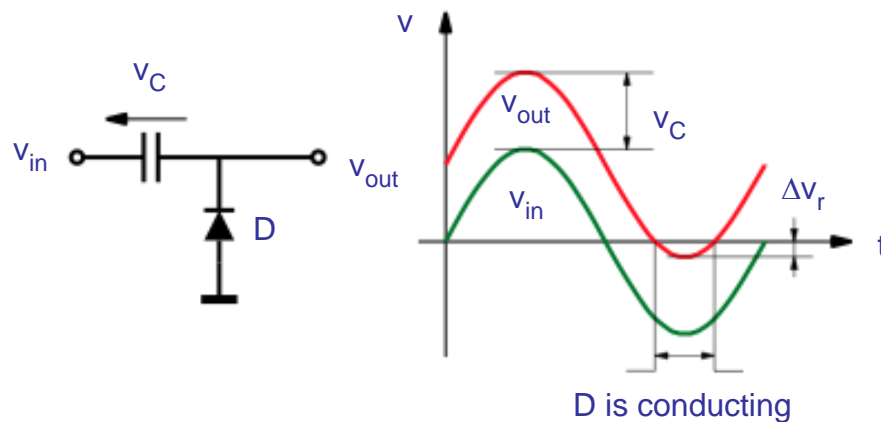


Peak detector

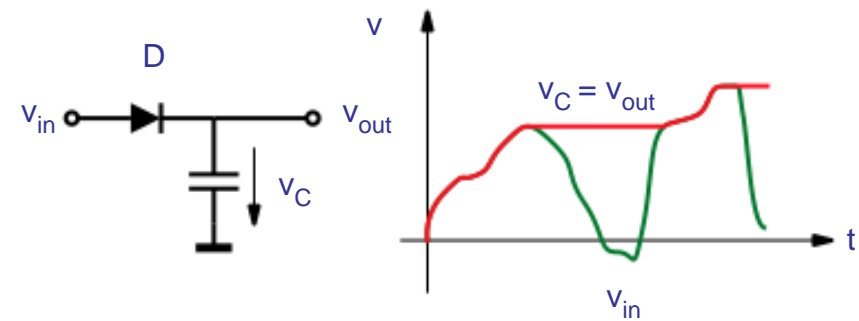


From low-voltage AC to high-voltage DC supply

Rectifier building blocks (2/2)


Voltage doubler

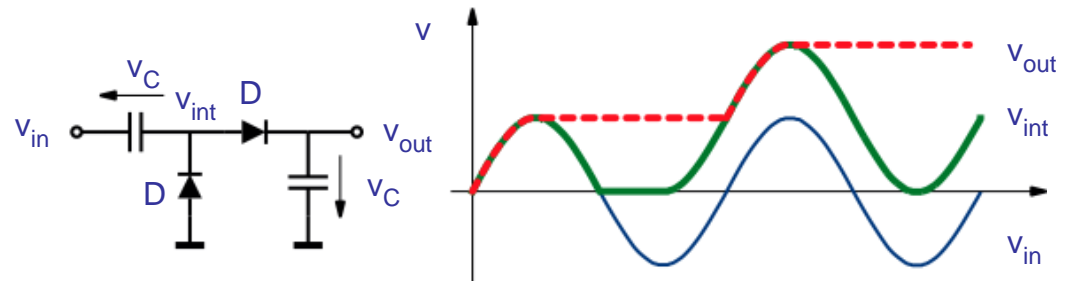

Full wave rectifier

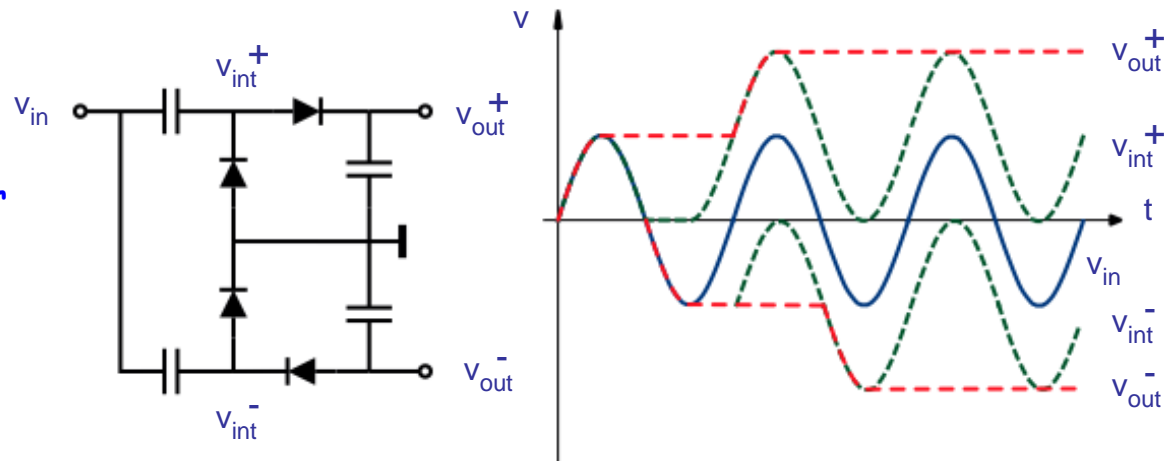

Rectifier Circuit (2 stage Greinacher)

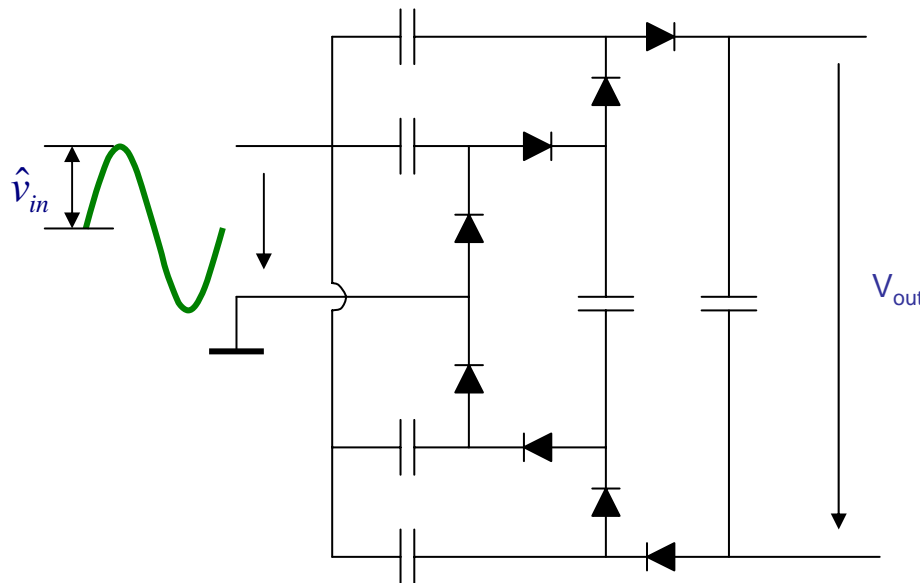


$$V_{out} = 4N\hat{v}_{in}$$

Where N is the number of stages

There is a need for a model taking into account

- The AC source v_{in} (antenna)
- The current delivered to the load
- Diodes non-idealities

Antenna Model

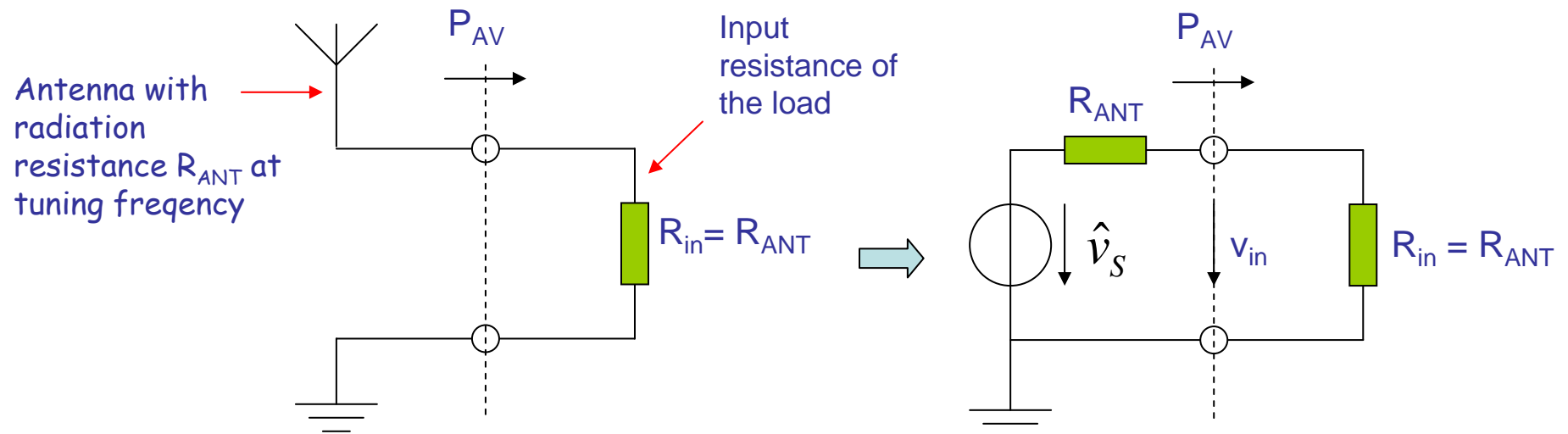

$$P_{AV} = \frac{\hat{v}_{in}^2}{2R_{in}}$$

→ At load matching conditions ($R_{ANT} = R_{IN}$)

$$\hat{v}_S = 2\hat{v}_{in} = 2\sqrt{2 \cdot P_{AV} \cdot R_{ANT}}$$


Rectifier input voltage: influence of R_{in}

The voltage amplitude \hat{v}_{in} at the rectifier input is given by:

$$\hat{v}_{in} = 2\sqrt{2P_{AV}R_{ant}} \frac{R_{in}}{R_{in} + R_{ant}}$$

To maximize \hat{v}_{in} and Power:

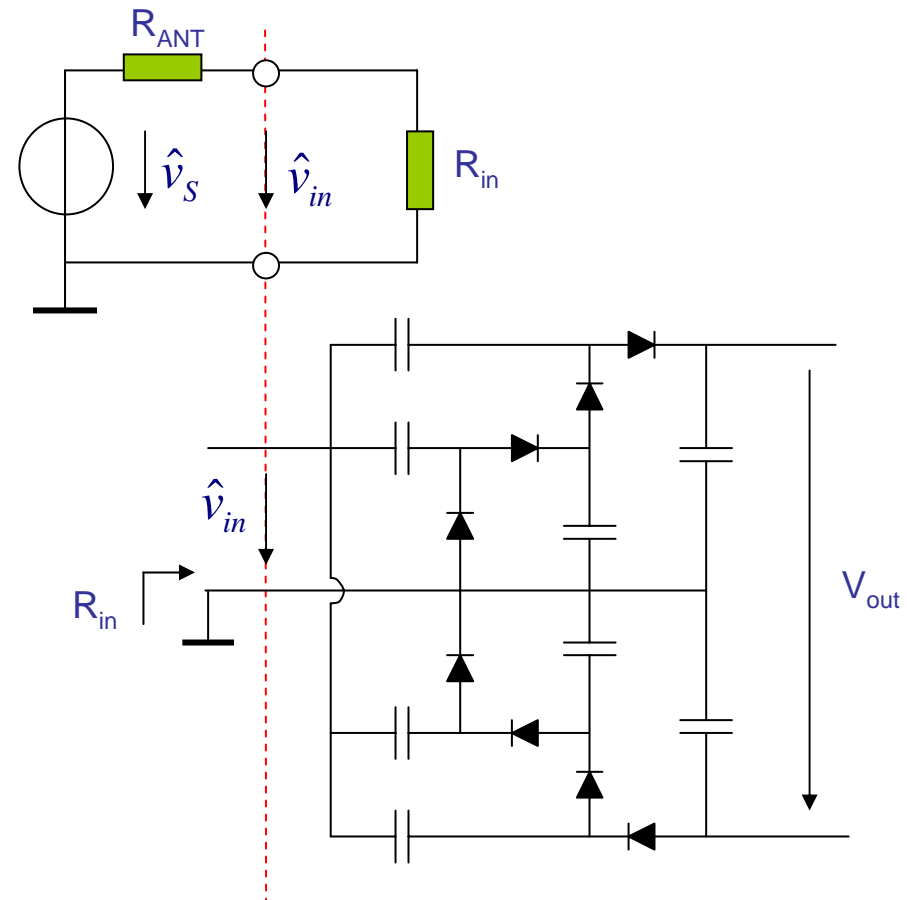- Maximize R_{ant}
- Keep R_{in} equal to R_{ant}




2 Wireless Power Transmission


Issue
Model
Results
Impacts on RFID Systems



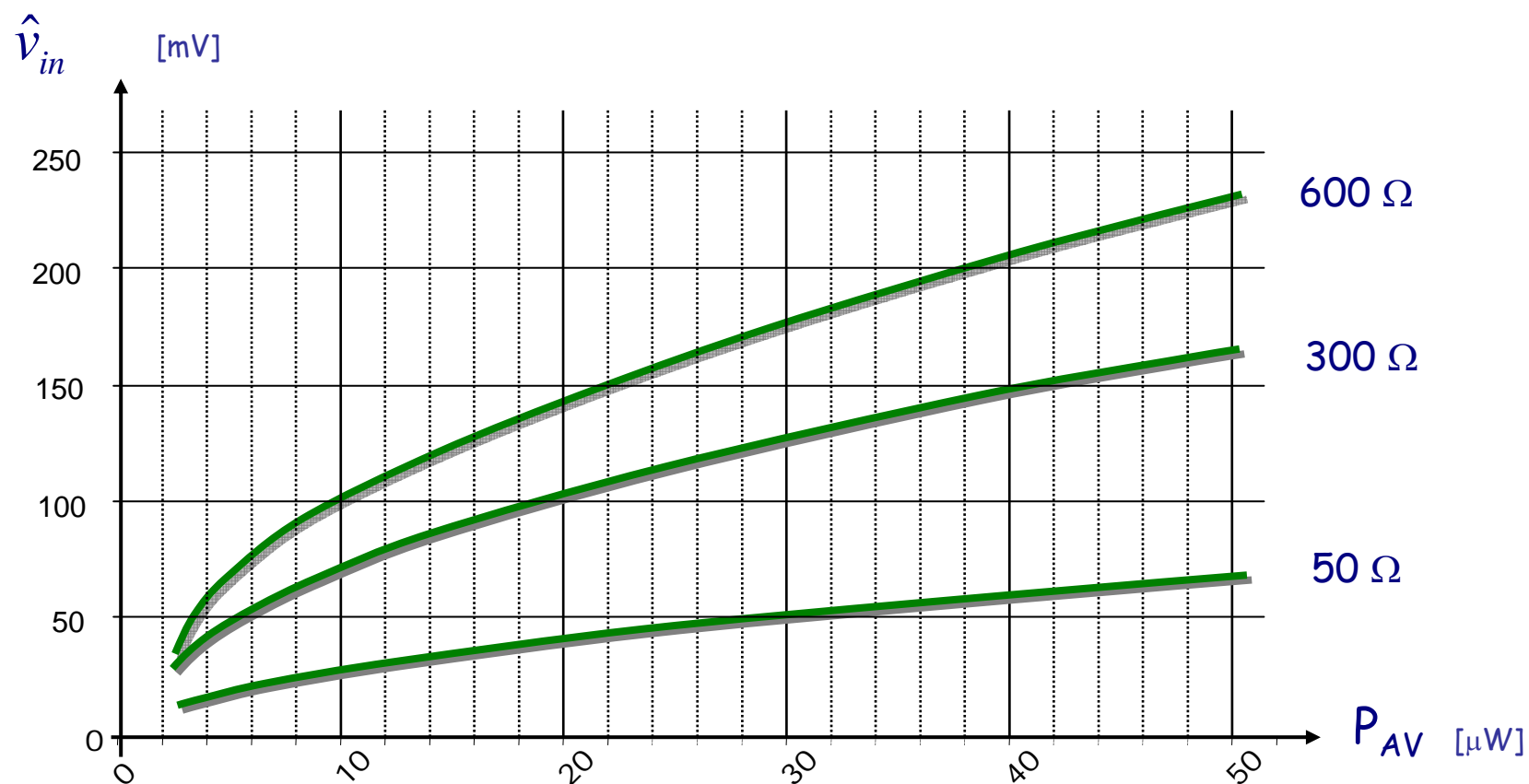Rectifier input voltage for $R_{ANT} = R_{in}$



Rectifier Equivalent Circuit Model

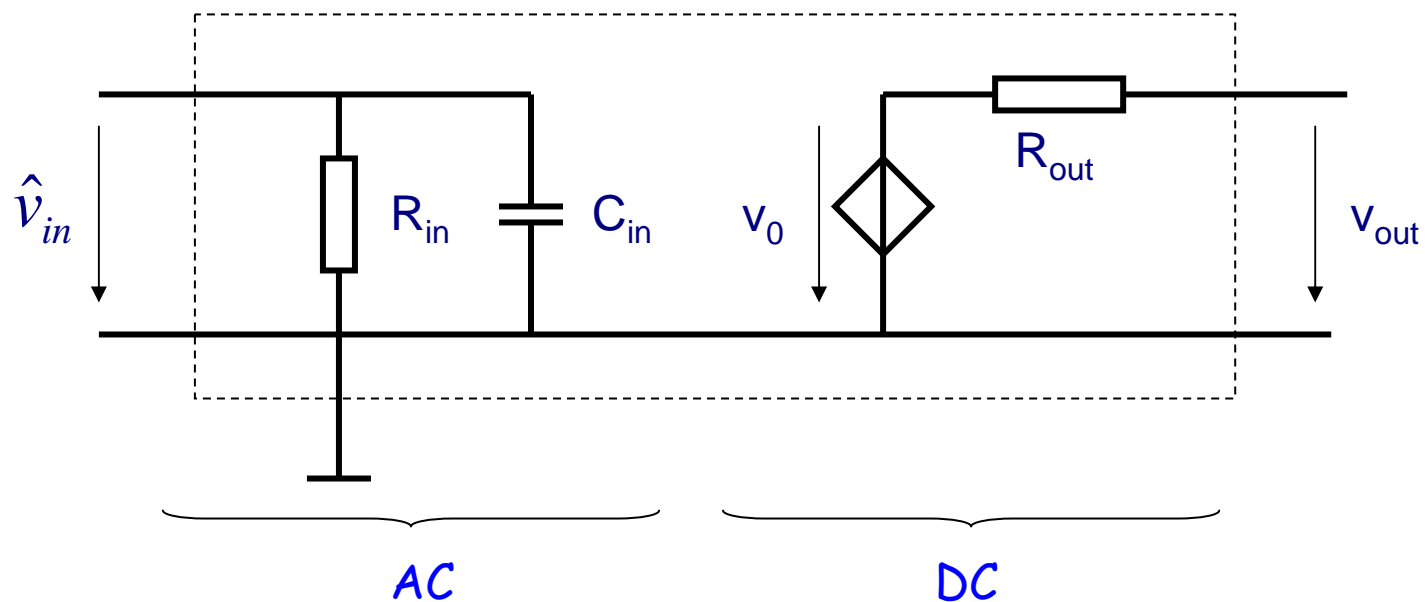

Assumptions

- The rectifier operates in steady-state mode;
- The output current is constant;
- All diodes are identical;
- The coupling capacitors are considered as short-circuits at the RF frequency
- The rectifier input current is transformed into an equivalent sinusoidal current

Model Derivation (steady state conditions)

1. Ideal diodes


$$\int_0^T i_C(t) dt = 0 \quad \text{For all capacitors}$$

$$\Rightarrow \int_0^T i_D(t) dt = I_{out} \cdot T \quad \text{For all diodes}$$

$$\overline{P}_{in} = \frac{1}{T} \cdot \int_0^T v_{in}(t) \cdot i_{in}(t) dt = \frac{\hat{v}_{in}^2}{2 \cdot R_{in}}$$

also
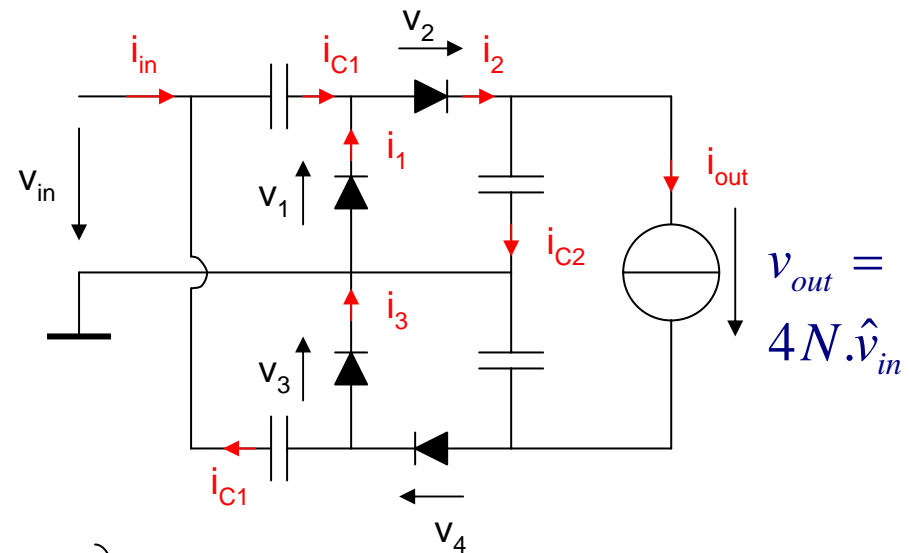
$$\overline{P}_{in} = P_{out,DC} = V_{out} \cdot i_{out} = 4N \cdot \hat{v}_{in} \cdot i_{out}$$



$$\Rightarrow R_{in} = \frac{\hat{v}_{in}}{8N I_{out}}$$

Model Derivation (steady state conditions)


2. Real diodes

$$\int_0^T i_C(t) dt = 0 \quad \text{For all capacitors (1)}$$

$$\Rightarrow \int_0^T i_D(t) dt = I_{out} \cdot T \quad \text{For all diodes (2)}$$

$$\text{with } i_D(t) = F[v_D(t)] \quad \text{Real diode characteristic (3)}$$
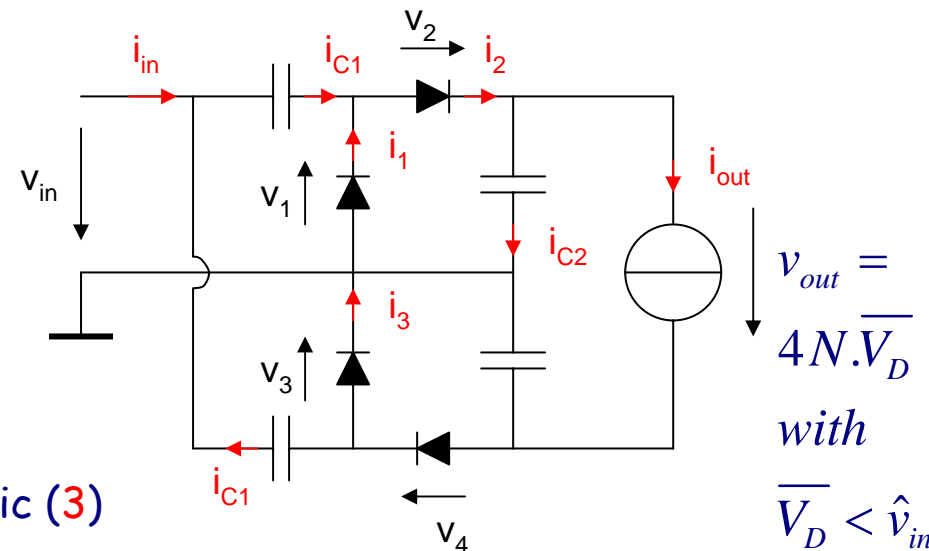
$$\text{and } v_D(t) = \overline{V}_D \pm \hat{v}_{in} \cdot \sin \omega t \quad (4)$$





- V_D is obtained by solving (1), (2), (3)

- It can be shown that

$$v_{out} = 4N \cdot \overline{V}_D$$


Model Derivation (detail)

Ideal Diodes vs. Real Diodes

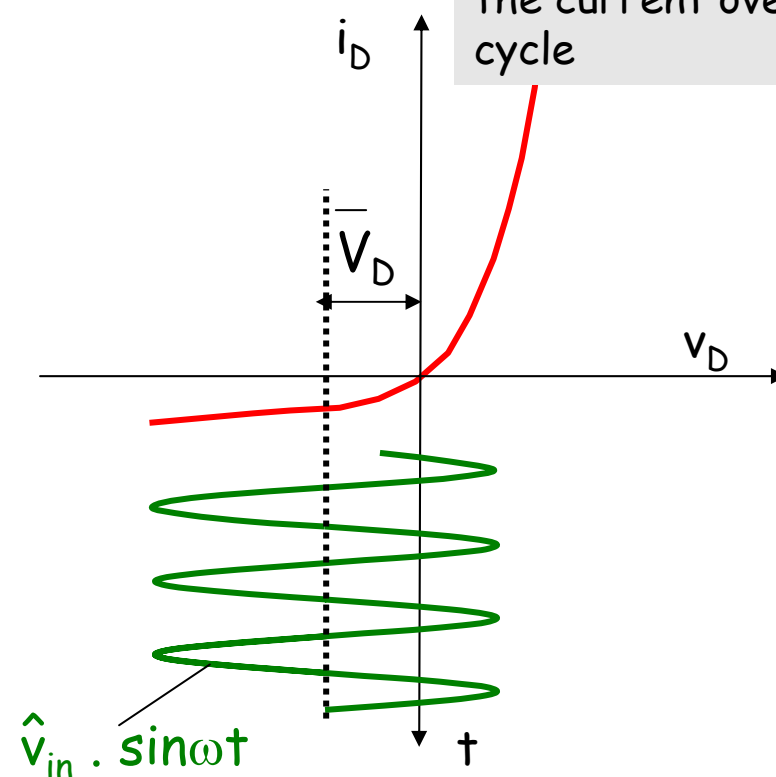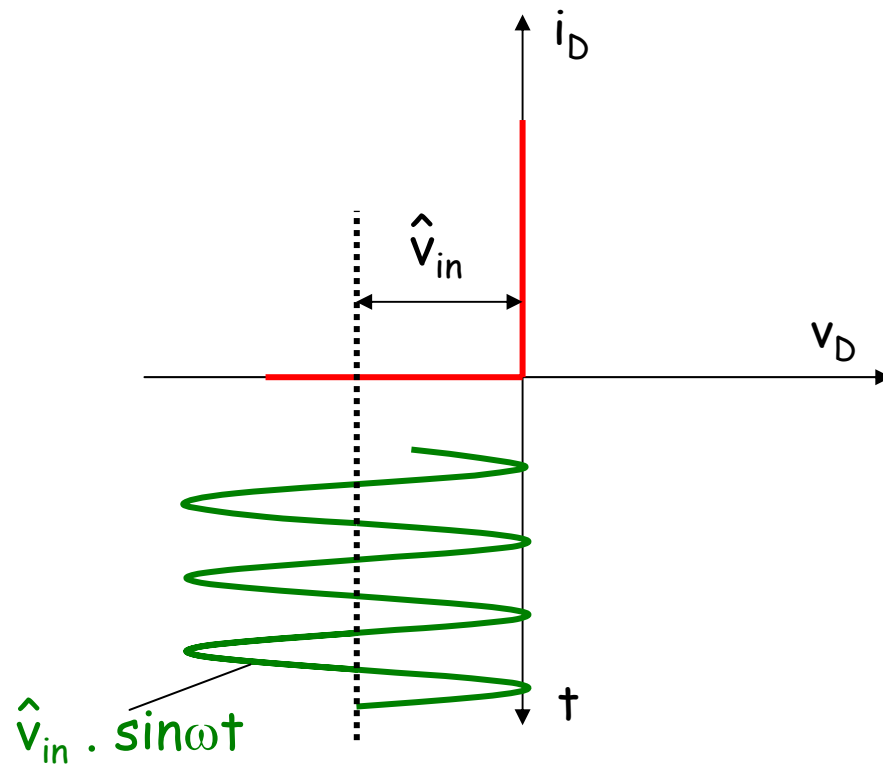


With real diodes, V_D must be lower than \hat{v}_{in} to get a positive balance of the current over one cycle

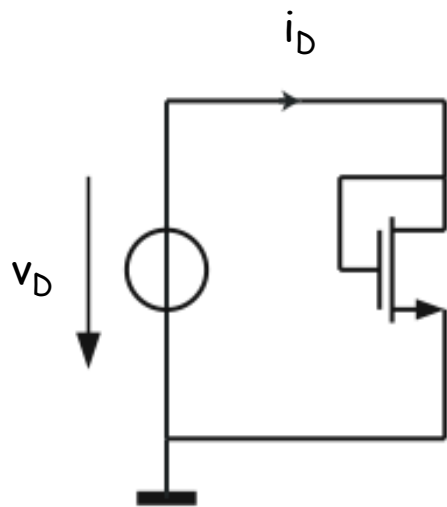Current/Voltage characteristics of MOS diodes



Diode mounted transistor

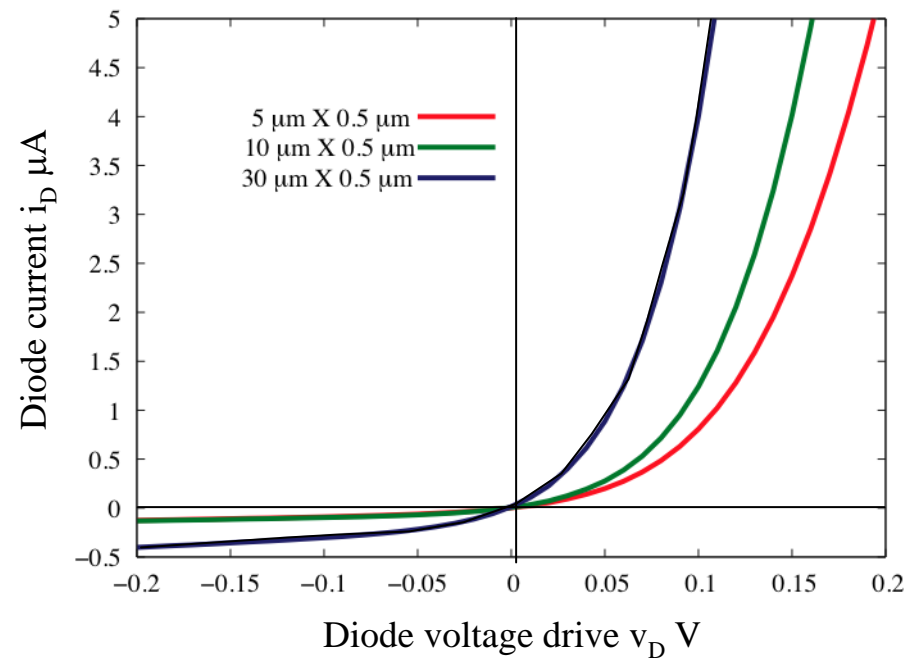Current-voltage characteristics of typical measured device



Determination of R_{in} (Real diodes)

- R_{in} models the power that enters the circuit:

$$P_{in} = \frac{1}{T} \int_0^T v_{in} i_{in}(t) dt = \frac{4N}{T} \int_0^T v_{in} i_D(t) dt$$

- The mean power can also be calculated using the usual relation:

$$P_{in} = \frac{\hat{v}_{in}^2}{2R_{in}} \quad \Rightarrow \quad R_{in} = \frac{\hat{v}_{in}^2}{\frac{8N}{T} \int_0^T v_{in} i_D(t) dt}$$

- Based on the I/V characteristic of a *single diode*, we can compute the power-equivalent input resistance R_{in}

Determination of C_{in}

- Our approach to calculate C_{in} is to compute the mean capacitance over one period of time:


$$C_{in} = \frac{4N}{T} \int_0^T C_D \left[\overline{V_D} + \hat{v}_{in} \sin \omega t \right] dt$$

where $\overline{V_D}$ is the constant voltage that appears on each diode during steady-state

- Based on the C/V characteristic of a *single diode*, we can compute the equivalent input capacitance C_{in}

Measurements & Comparisons

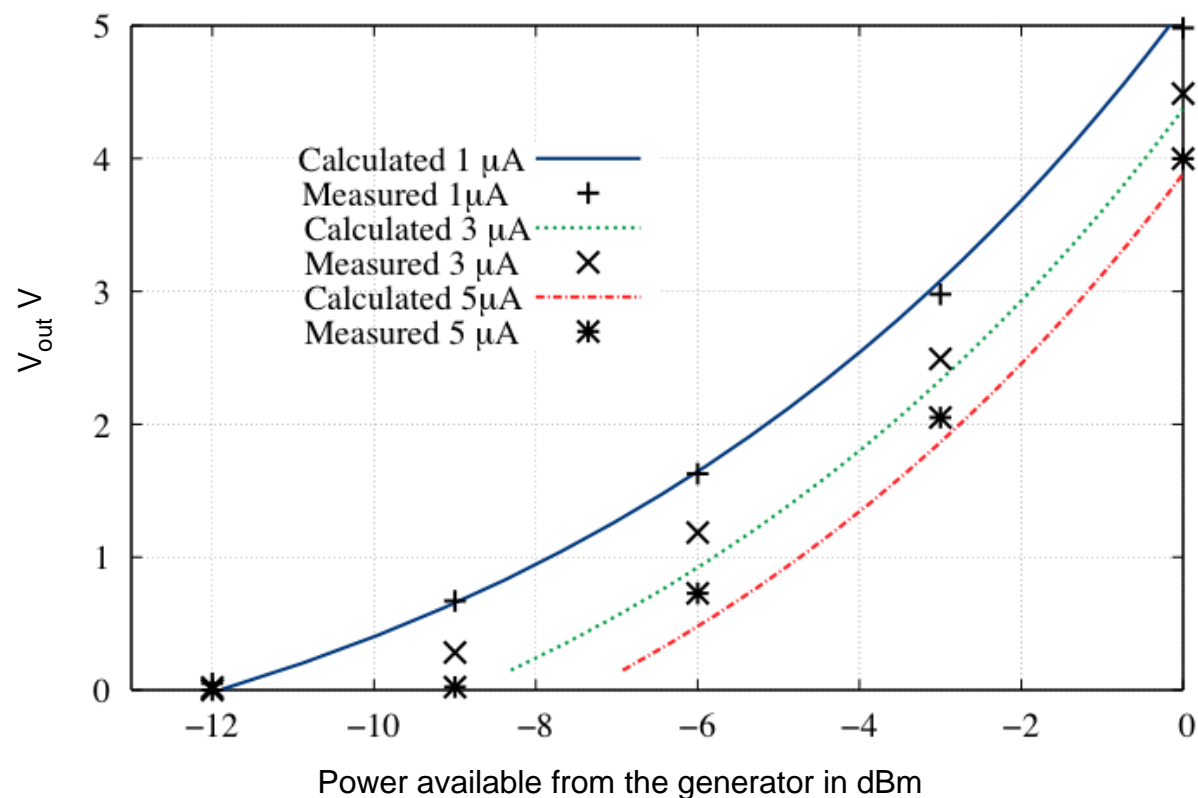Output voltage vs Input Power (50Ω, 900 MHz), 0.5μm SOS Techno



Model possibilities

The model allows a reasonably accurate prediction of:

- The output voltage (V_o)
- The input impedance (R_{in}, C_{in})
- The output resistance
- The conversion efficiency

as a function of:

- The DC output Power / Current
- The antenna radiation resistance (R_{ant})
- The available power P_{AV} at the antenna
- The characteristics of the MOS diodes

3

Communication Issue

Analysis

Pseudo-PSK (pPSK)

Impacts on RFID Systems



3. COMMUNICATION ISSUES

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis

Pseudo-PSK (pPSK)

Impacts on RFID Systems



Modulation Types

The reflection coefficient at the tag-antenna interface can be varied in:

- Amplitude
- Phase

Two basic binary modulation types are possible: ASK & PSK

They must be compared in terms of

- Power available for both tag supply & for communication
- Communication quality (Bit Error Rate BER)

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis



Analysis

Pseudo-PSK (pPSK)


Impacts on RFID Systems



ASK modulation

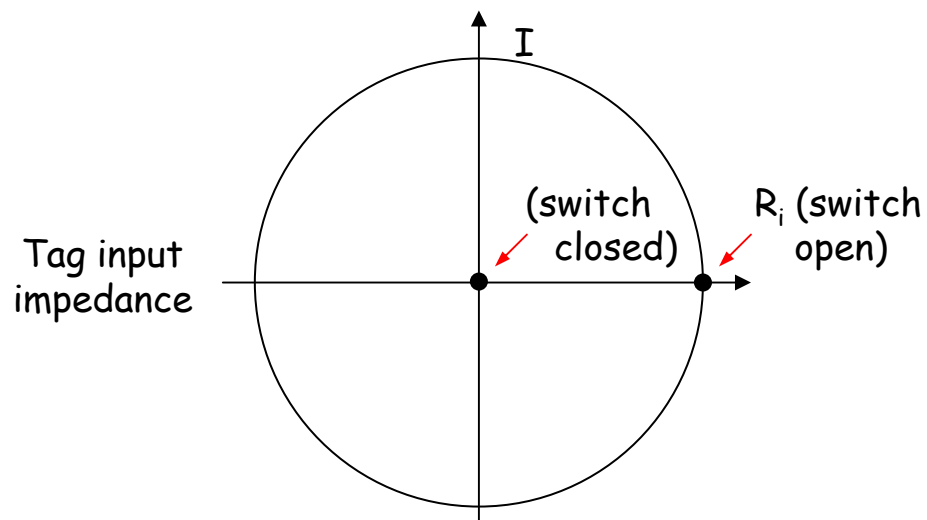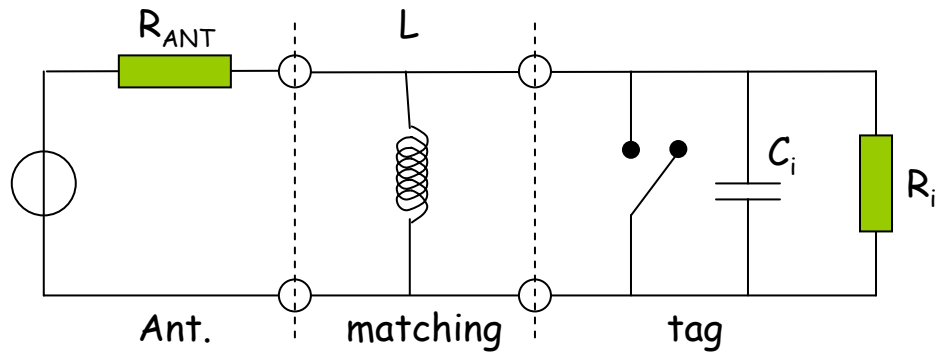

Reflected ASK modulated signal

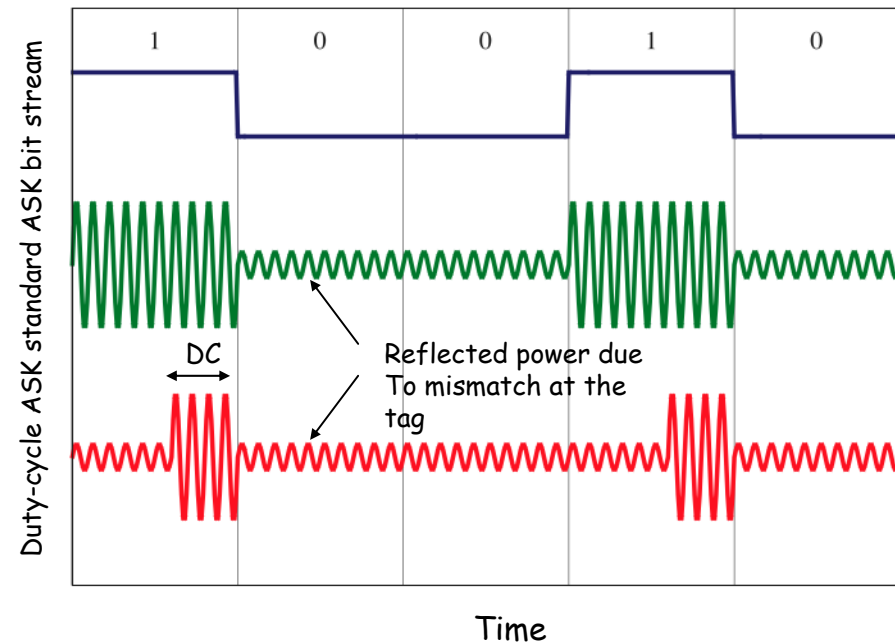

3 Communication Issue


- a Communication Analysis
- b Backscattering Analysis

Analysis

Pseudo-PSK (pPSK)
Impacts on RFID Systems





PSK modulation

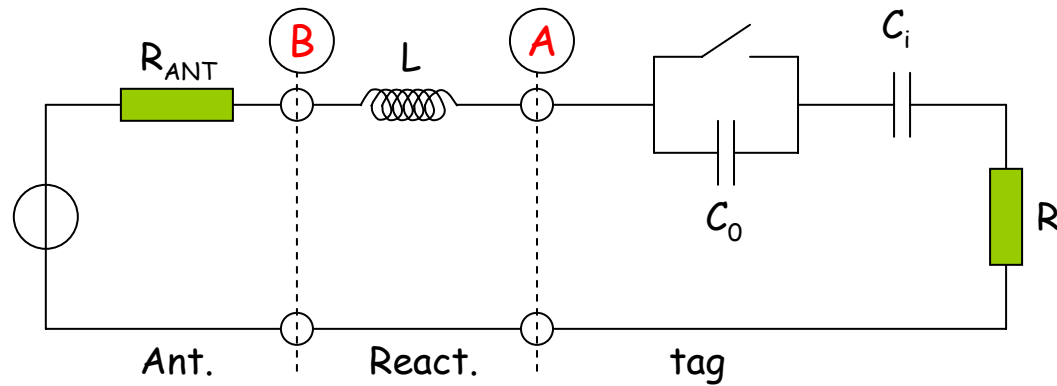

In **B**: Absorbed power
And reflected power
are constant

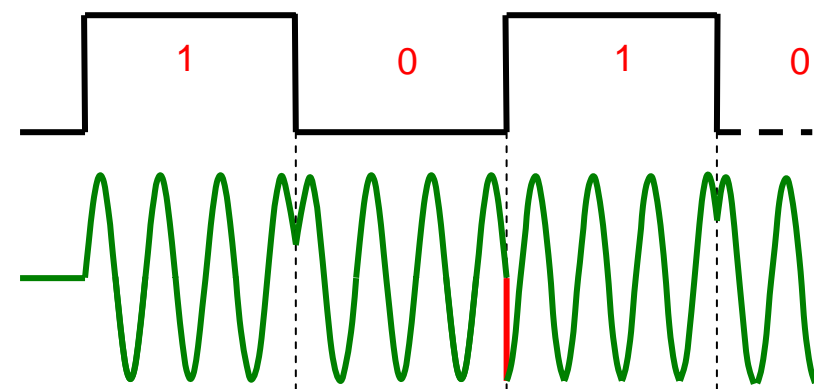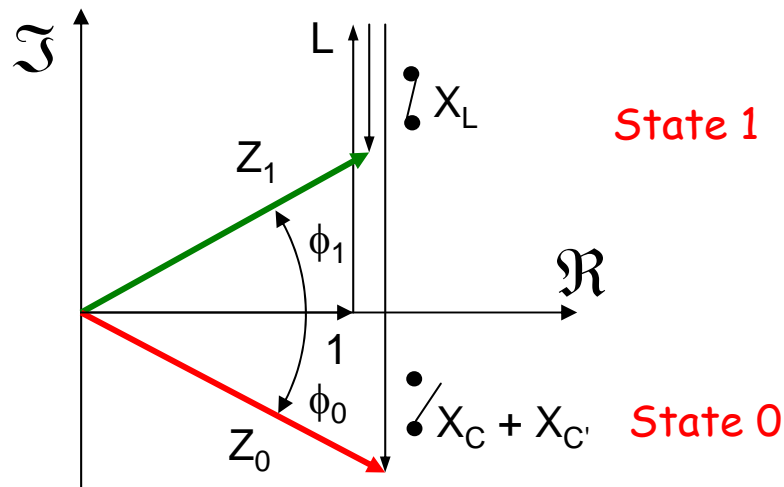In **A**: Voltage at tag input
is however **not** constant



Tag input impedance at B

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis

Pseudo-PSK (pPSK)

Impacts on RFID Systems



ASK / PSK Comparison

E_b = Average Energy per bit
 N_0 = Noise level at receiver input
 $\alpha = R_i / R_{ANT}$
 Q = tag input series Quality factor $1/\omega.R_i.C_i$
DC = Modulation Duty Cycle

ASK

$$BER = Q \left(\sqrt{\frac{E_b}{N_0} \cdot DC \cdot \left(-1 + \sqrt{\frac{(Q_{in}^2 + 1) \cdot (\alpha - 1)^2}{(\alpha + 1)^2 + Q_{in}^2 (\alpha - 1)^2}} \right)^2} \right)$$

PSK

$$BER = Q \left(\sqrt{2 \frac{E_b}{N_0} \cdot \frac{4 + \alpha(-8 + \alpha(4 + Q_{in}^2))}{4 + \alpha(8 + \alpha(4 + Q_{in}^2))} \cdot \sin \left(2 \arctan \left(\frac{4Q_{in}\alpha}{-4 + \alpha^2(4 + Q_{in}^2)} \right) \right)^2} \right)$$

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis


Analysis

Pseudo-PSK (pPSK)

Impacts on RFID Systems



ASK / PSK Comparison

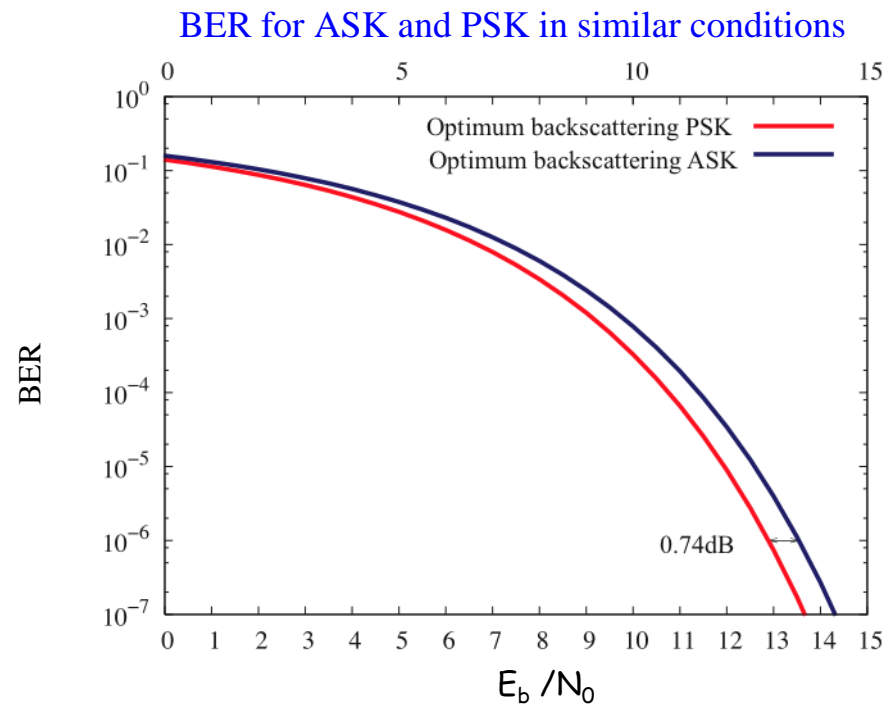

Optimal ASK and PSK BER comparison
(ASK: DC = 100%, $\alpha = 1$ and PSK: $\alpha = 1$, $Q_{in} = 5.6$)

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis

Pseudo-PSK (pPSK)

Impacts on RFID Systems



Tag input impedance for long-distance RFID

Reflection coefficient amplitude

Priority is given to communication distance vs. data rate


The real part of R_{in} is very high ($\gg 1k\Omega$) and much higher than R_{ant}

Reflection coefficient is close to ± 1

The input capacitance is equal to a few hundreds fF

Matching conditions

$$\Gamma = 0 \text{ and } \alpha = 1$$

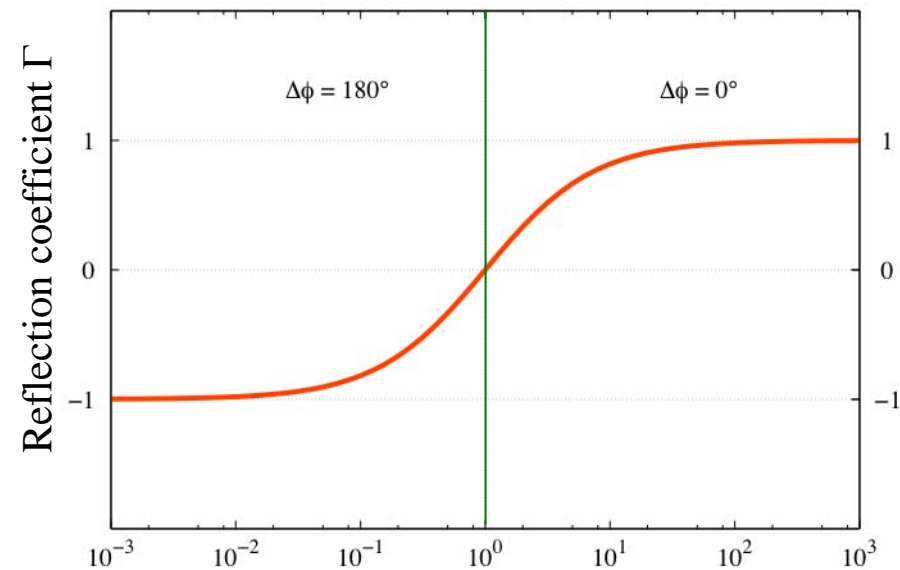

Normalized resistance $\alpha = R_{in} / R_{ant}$

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis

Pseudo-PSK (pPSK)



Impacts on RFID Systems



Pseudo - PSK

In practice $R_i > R_{ANT}$
(~1 order of magnitude)

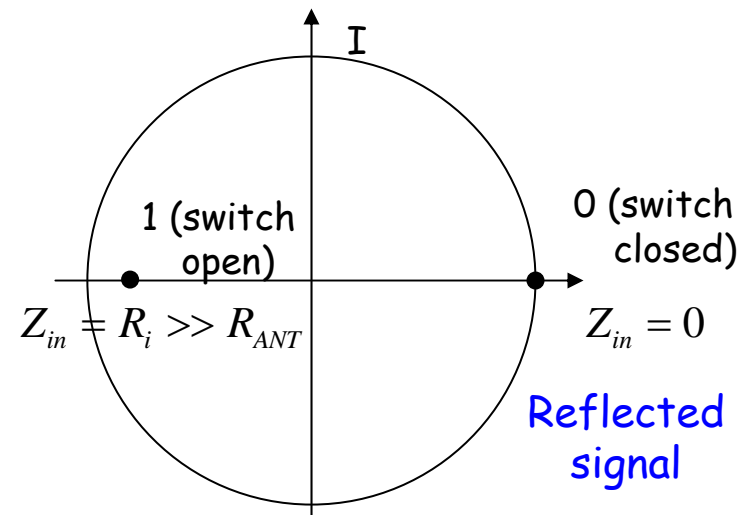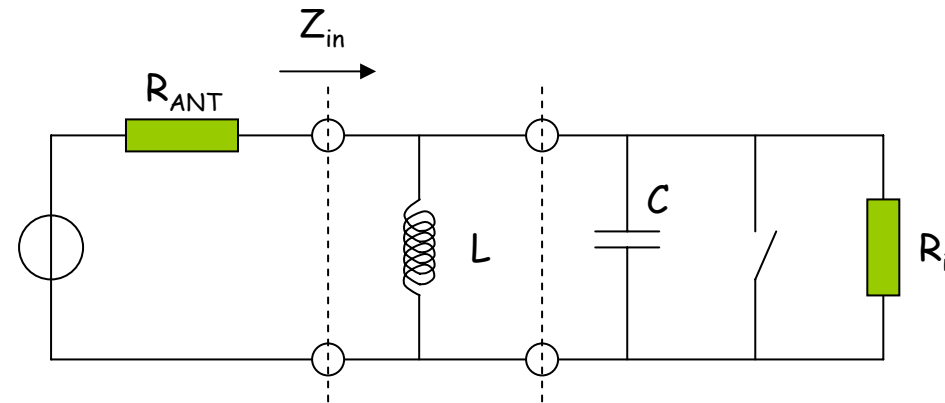- Absorbed power is lower than ideal
- Voltage available at rectifier input is higher
- Modulation is very efficient with a 180° phase shift



3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis


Pseudo-PSK (pPSK)

Impacts on RFID Systems



Power waves

Power waves for both modulation states

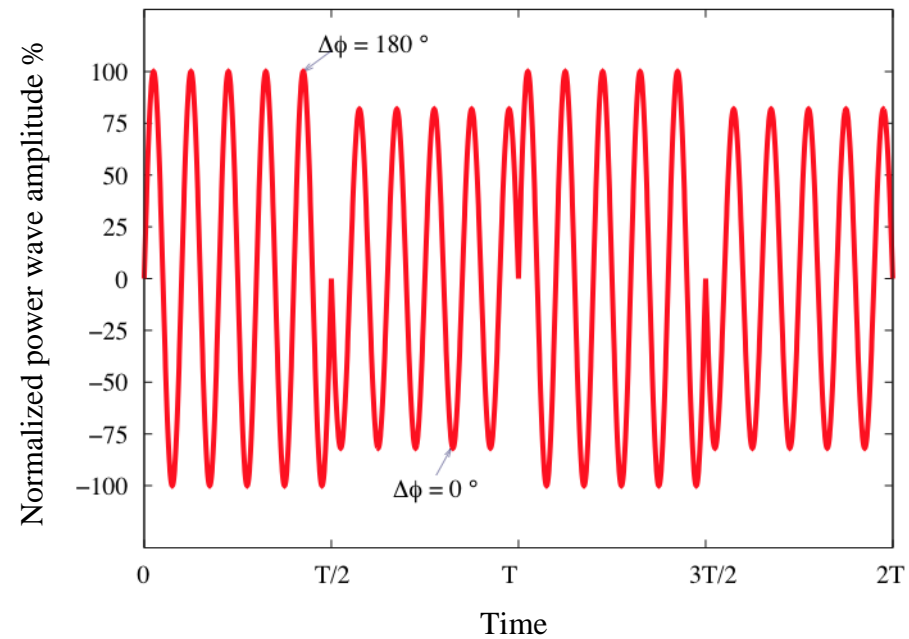

3 Communication Issue

- a Communication Analysis
- b Backscattering Analysis

Analysis


Pseudo-PSK (pPSK)

Impacts on RFID Systems



Modulation Type Comparison

ASK, PSK & pPSK comparison

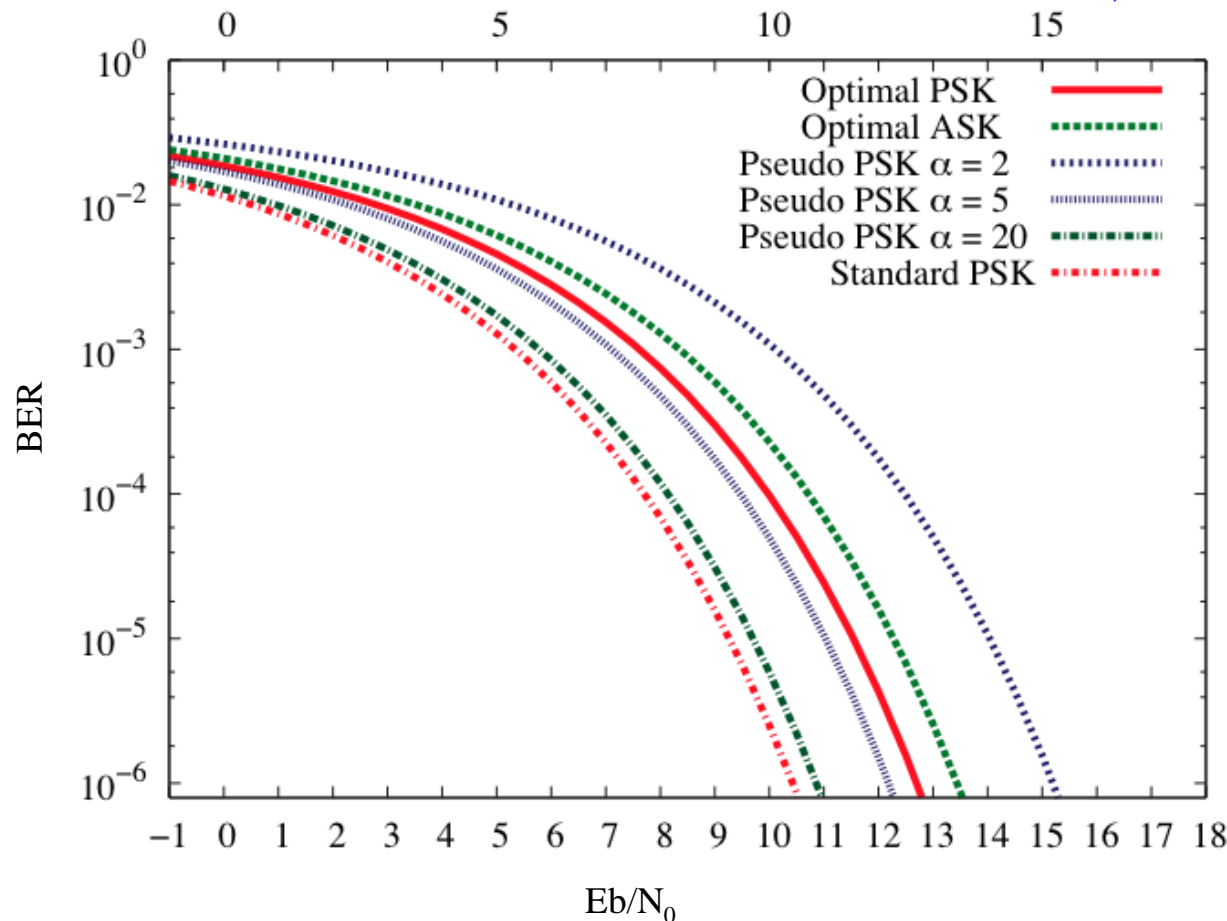

Pseudo-PSK is an excellent trade-off considering the high impedance level of the tag RF front-end in this application

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications

Technology

Architecture

Results and Comparison



4. TAG AND READER DESIGN

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications

Technology

Architecture

Results and Comparison



Initial Specifications for the tag IC

Parameter	Value
Frequency range	2.40 - 2.48 Ghz
Reader P_{EIRP}	4 W
Tag power	$\approx 1 \mu W$
Operating distance	> 5 m
Reader to tag	AM (OOK) modulation
Tag to reader	p-PSK modulation
Data rate	≥ 10 kbps

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications

Technology

Architecture

Results and Comparison



Technological Issues

Desired features

- Low- V_T rectifying devices \rightarrow start-up voltage
- Steep subthreshold slope \rightarrow efficiency
- Overall excellent RF behaviour \rightarrow μ wave operation

Selected technology

PEREGRINE 0.5 μ m FD SOS Technology

Gate oxide thickness : 10 nm

Silicon layer thickness : 100 nm

3 V_T 's available for both N-channel & P-channel transistors

$F_{T,typ} = 14$ Ghz, $F_{MAX,typ} = 55$ Ghz @ $V_{DS}=1.5V$ & $I_D=5mA$ (n-chan.)

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture

Results and Comparison



Building Blocks

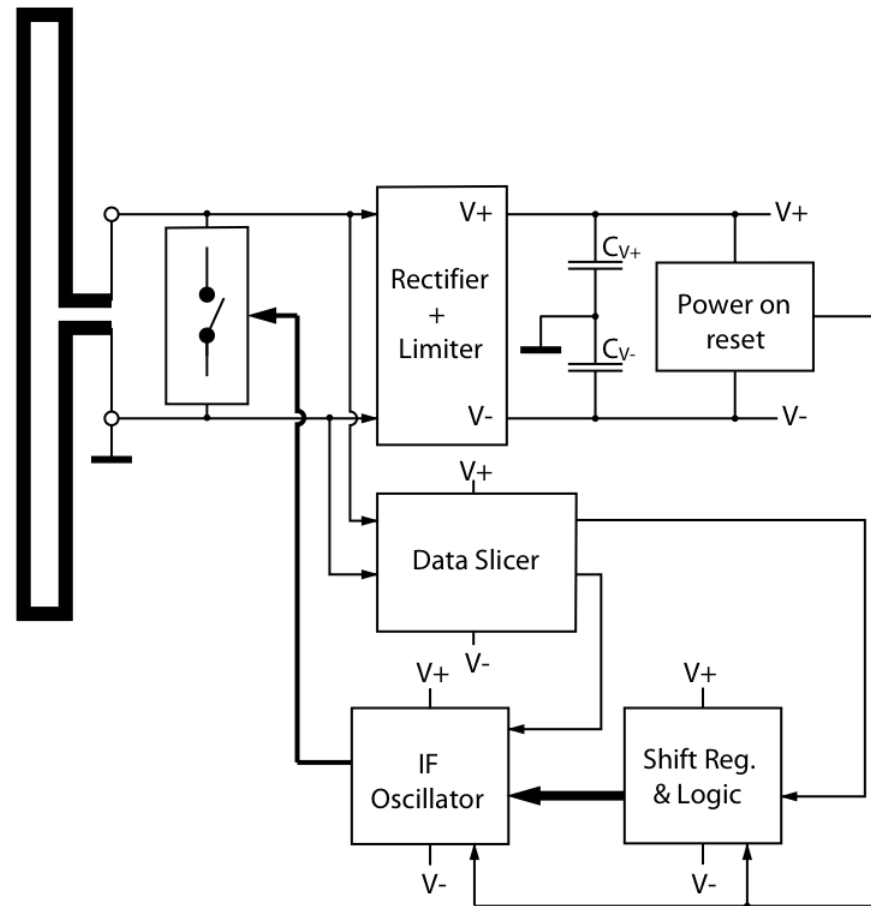

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture

Results and Comparison



Rectifier And Voltage regulation

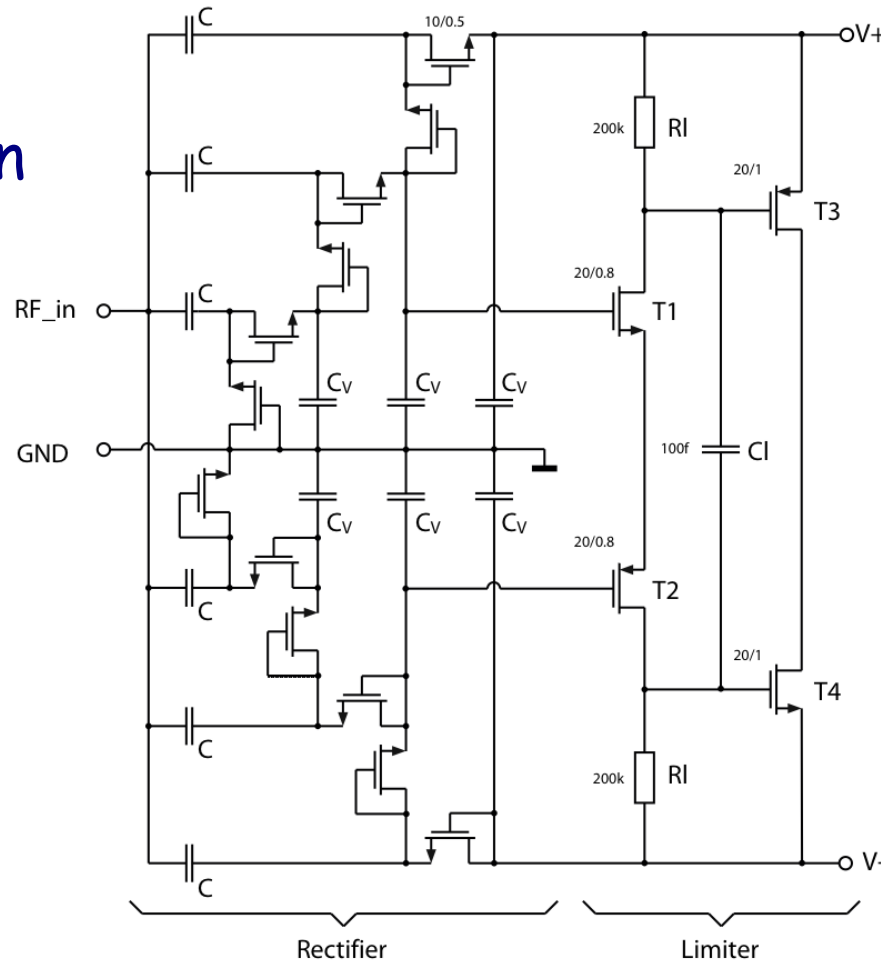

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture

Results and Comparison



Detector + signal conditioning

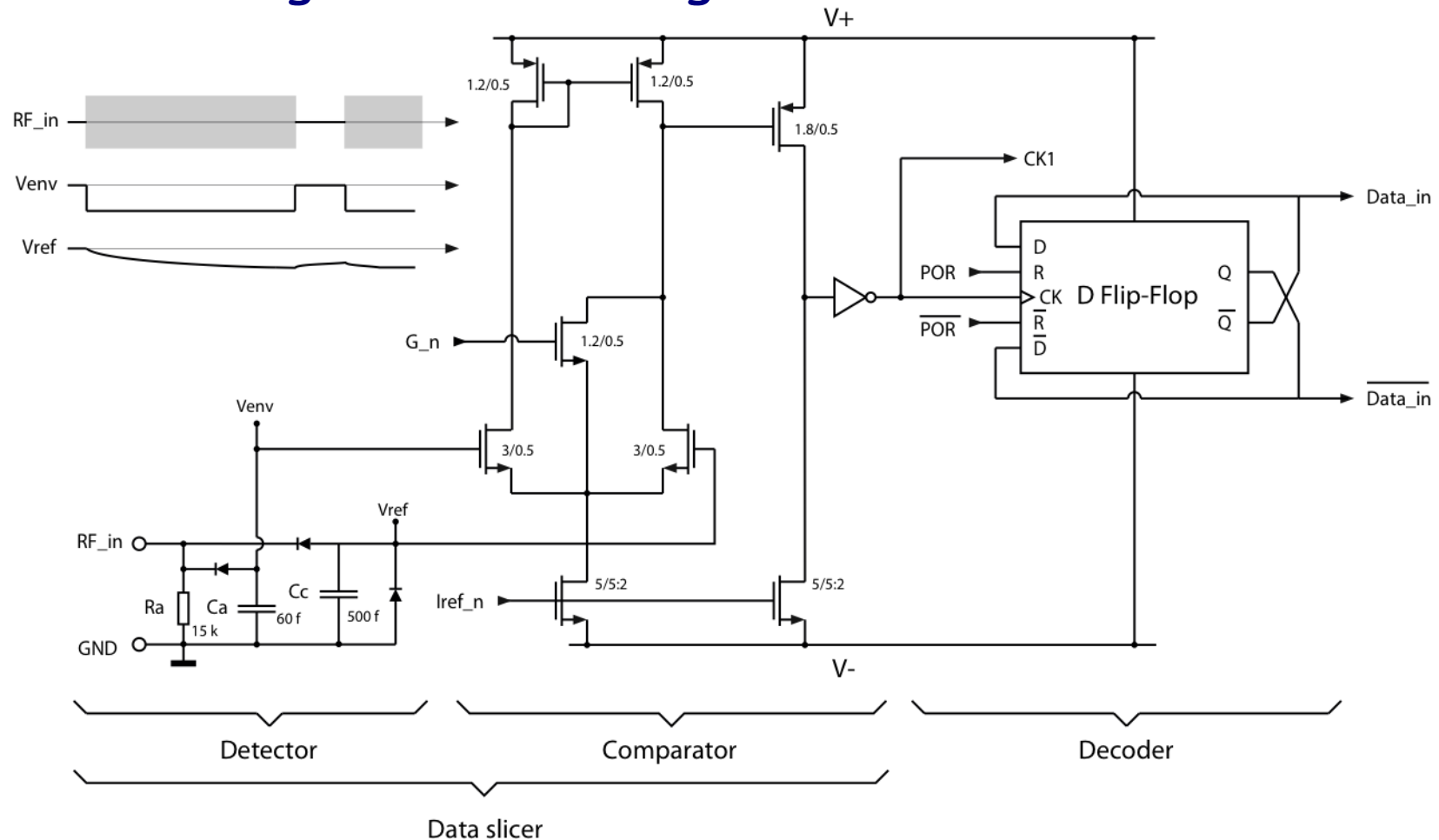

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture


Results and Comparison



IF Oscillator

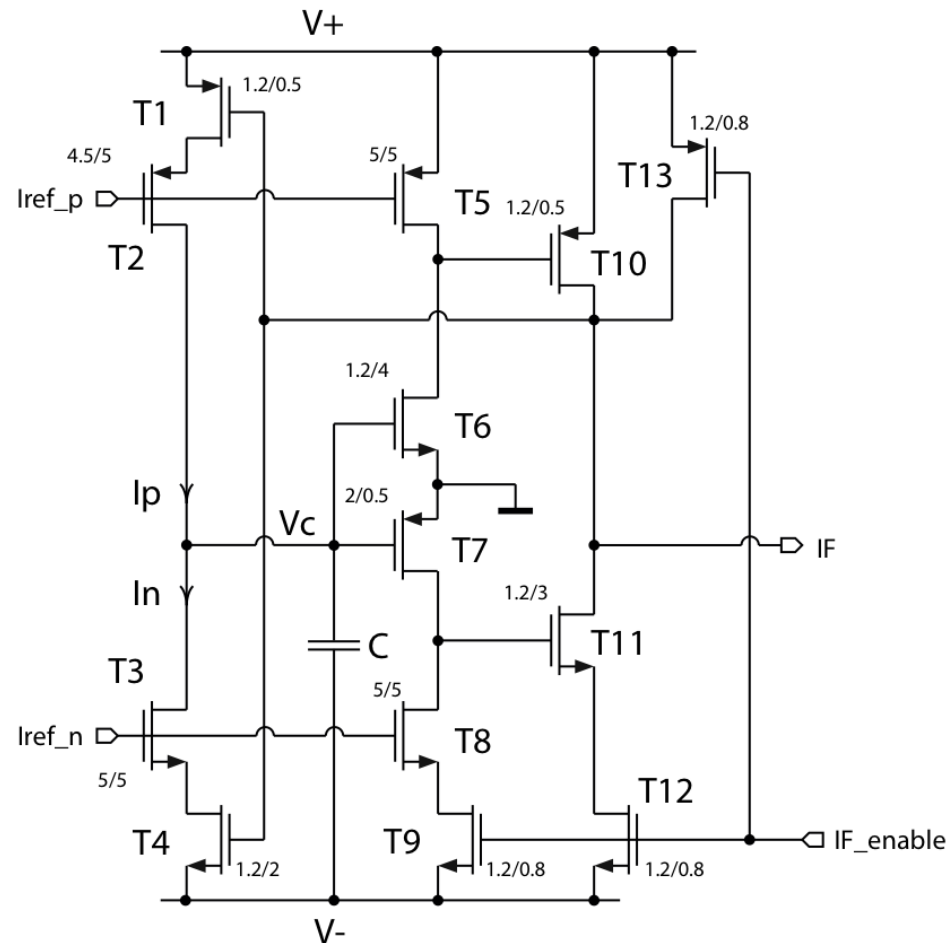

Modulator

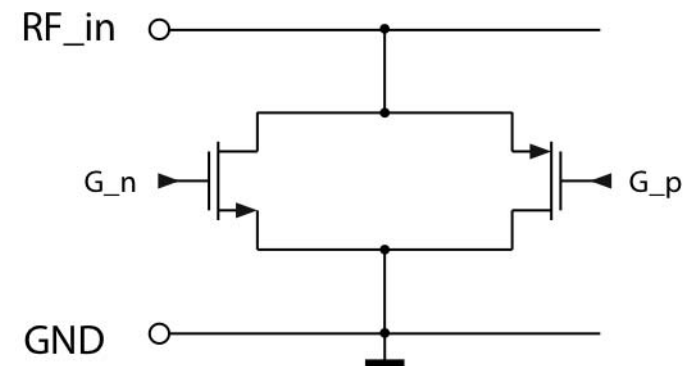

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture


Results and Comparison



Tag Die

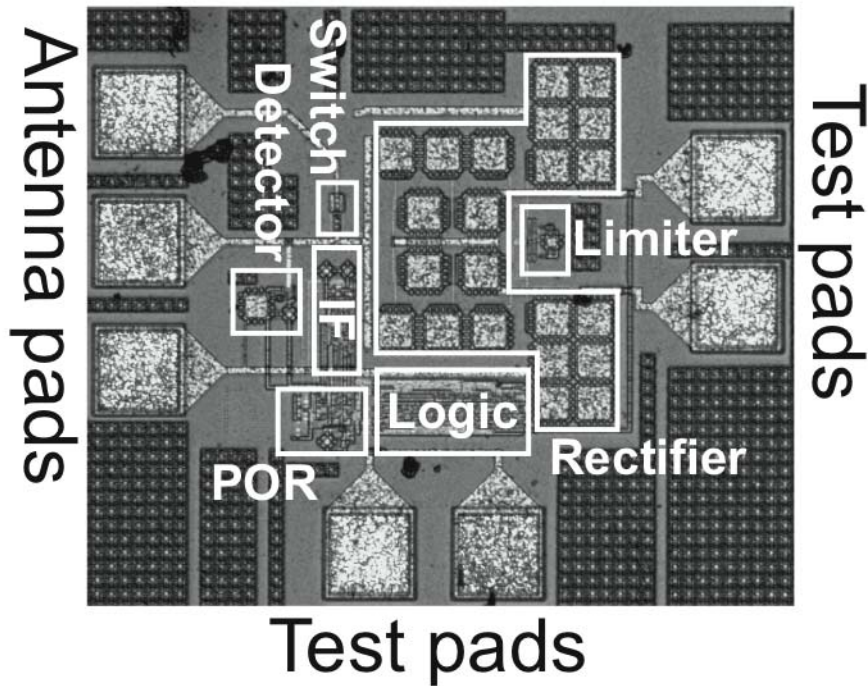

Complete Tag with antenna

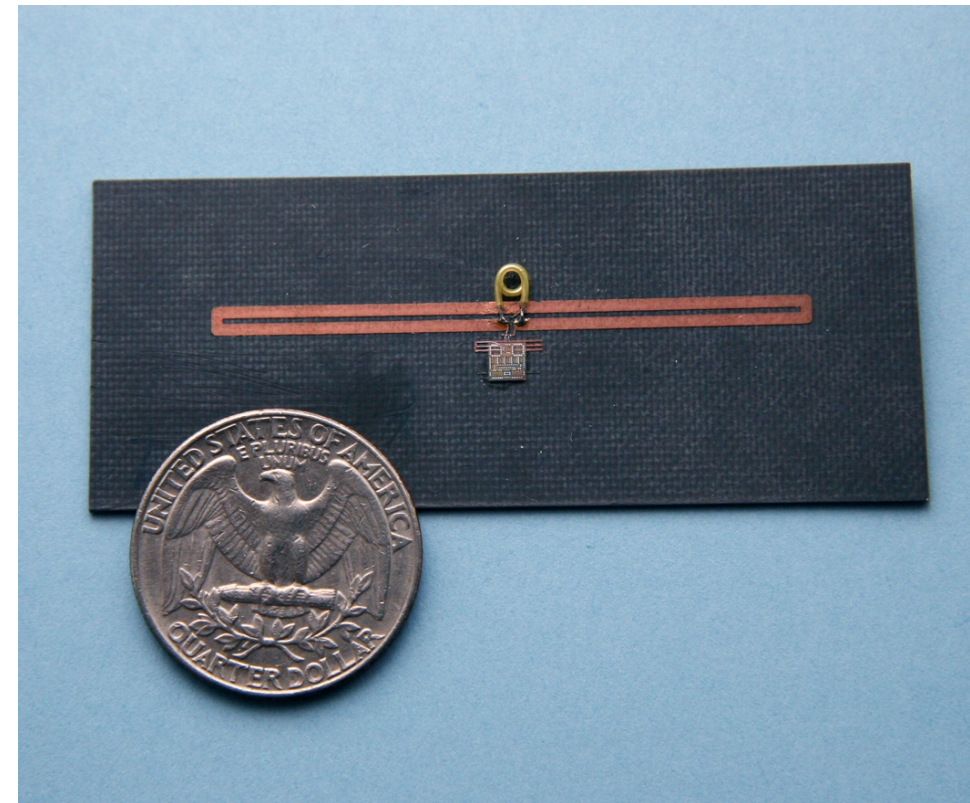

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications

Technology

Architecture

Results and Comparison



Reading Range

Frequency MHz	Antenna	Range m
2450	$\lambda/2$ -dipole	6
2450	$\lambda/2$ -dipole with inductive matching	9
2450	folded dipole	7
2450	folded dipole with inductive matching	12

At 12 m, the available power at the tag input is about $4.2 \mu\text{W}$ for a folded dipole (2dB gain)

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture

Results and Comparison



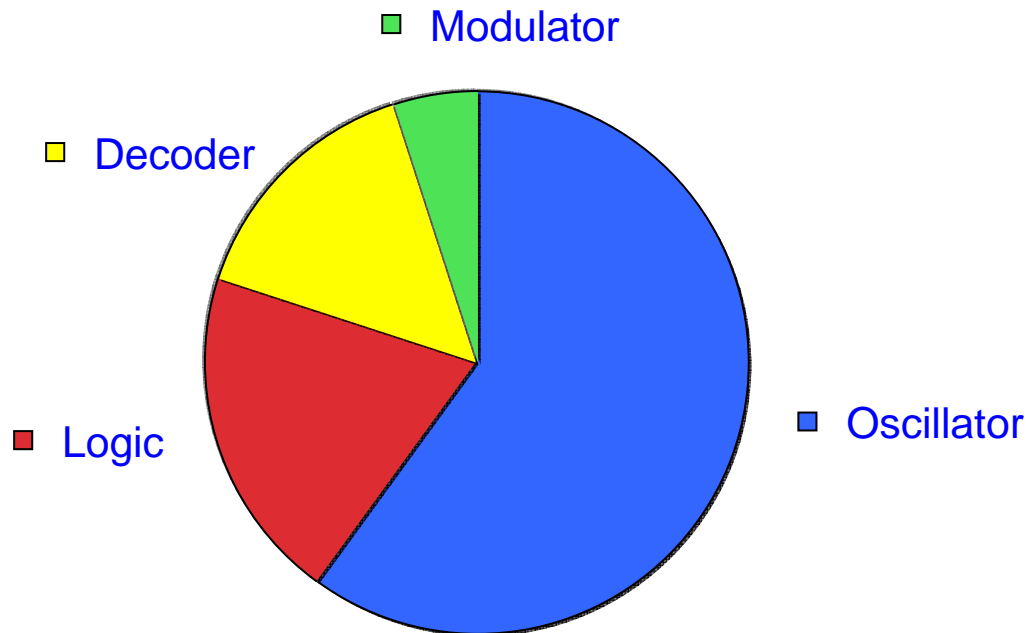Power distribution between tag components



Power management is the key issue !

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Specifications


Technology

Architecture

Results and Comparison



Tag consumption

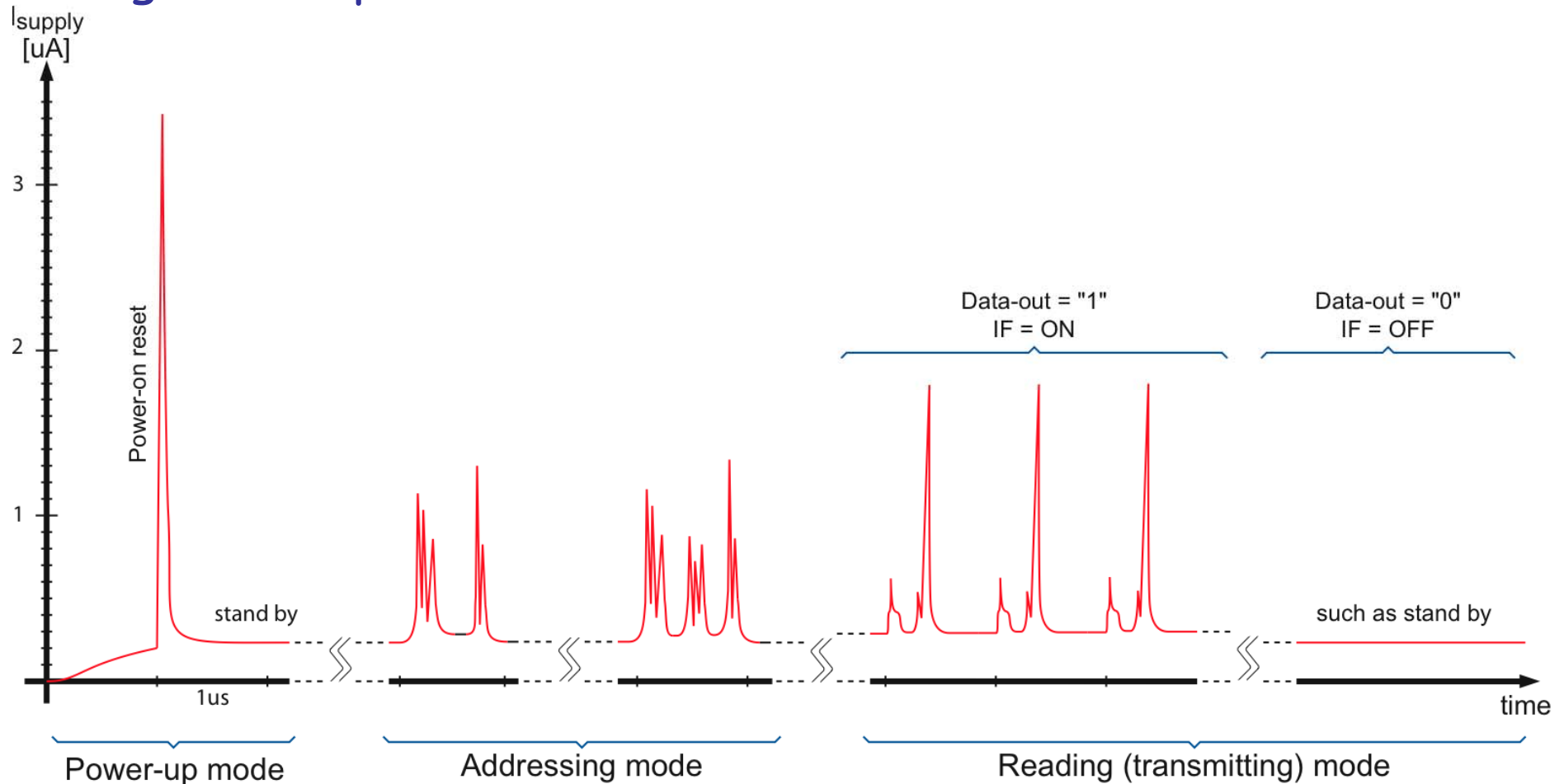

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design


Operational Principle

RF Processing

IF Processing



Basic RF Architecture

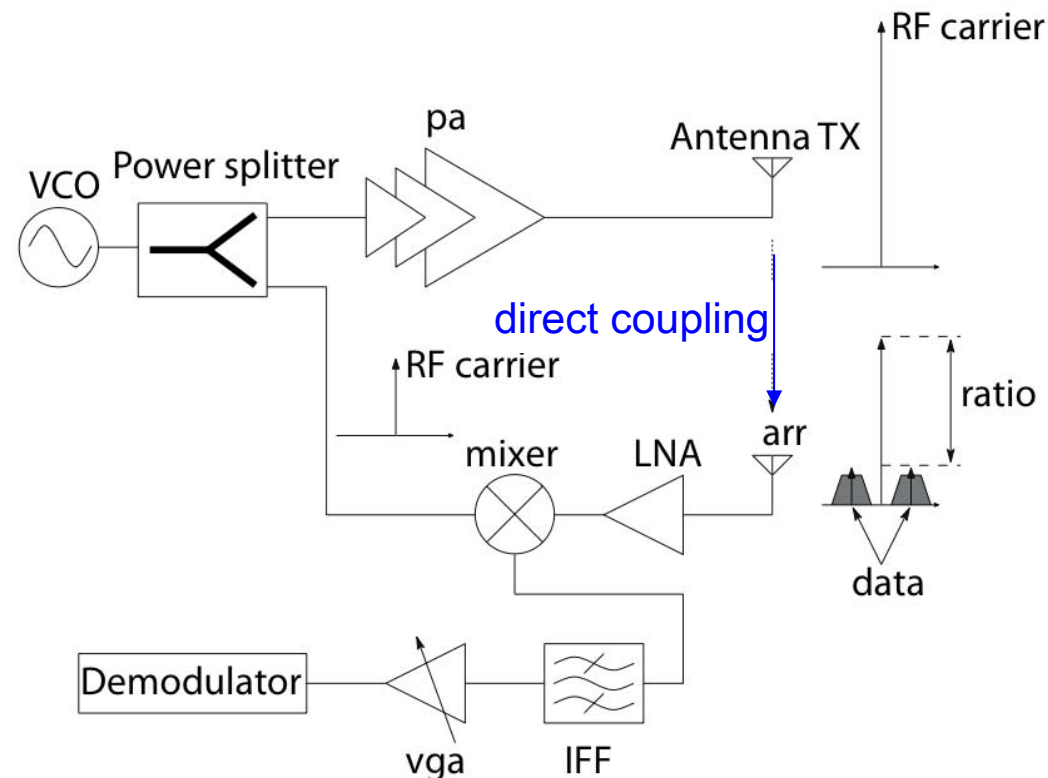

RF Front-end desensitization can occur due to direct-coupling effect
→ IP_3 issue

4 Tag & Reader Design

- a Tag Integrated Circuit Design
- b Reader Design

Operational Principle

RF Processing

IF Processing




Linearity or third order Interception Point $IP3$

It can be shown that

$$IIP3 \geq P_I + 4.8 \text{ (dBm)}$$

where :

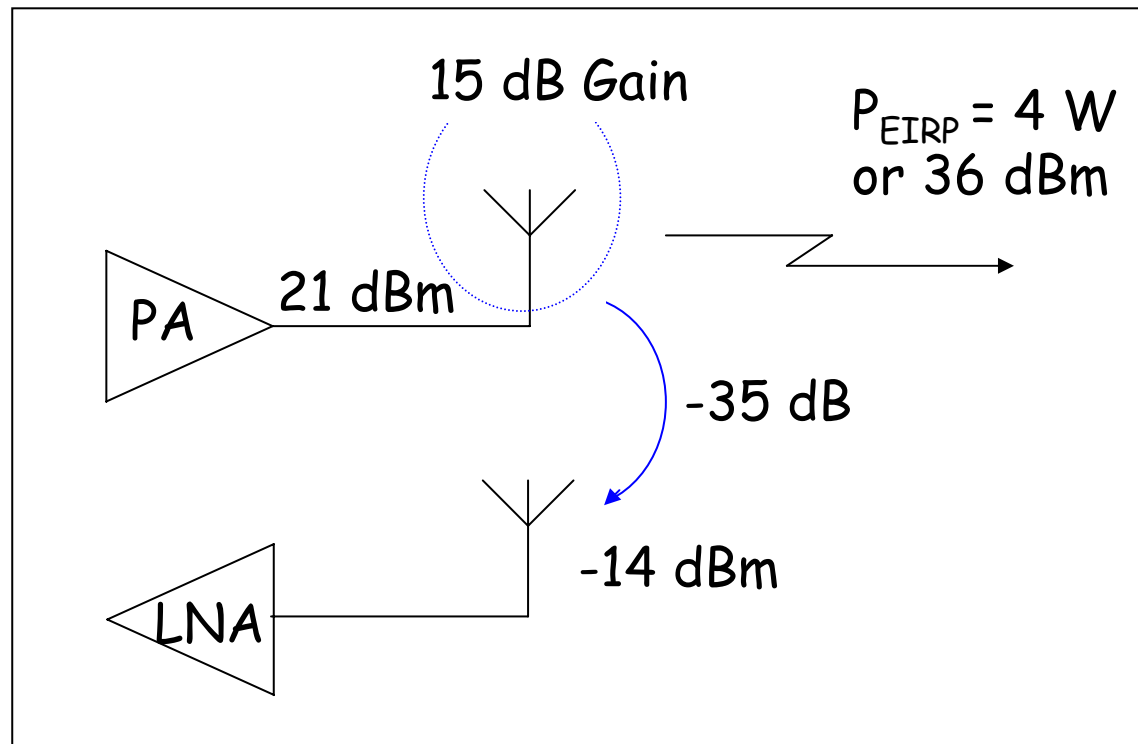P_I is the interferer power and
 $IIP3$ the System Input $IP3$



→ Spec. for overall system $IIP3$: $> -14 \text{ dBm} + 4.8 \text{ dBm} = -9.2 \text{ dBm}$

4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design


Operational Principle

RF Processing

IF Processing



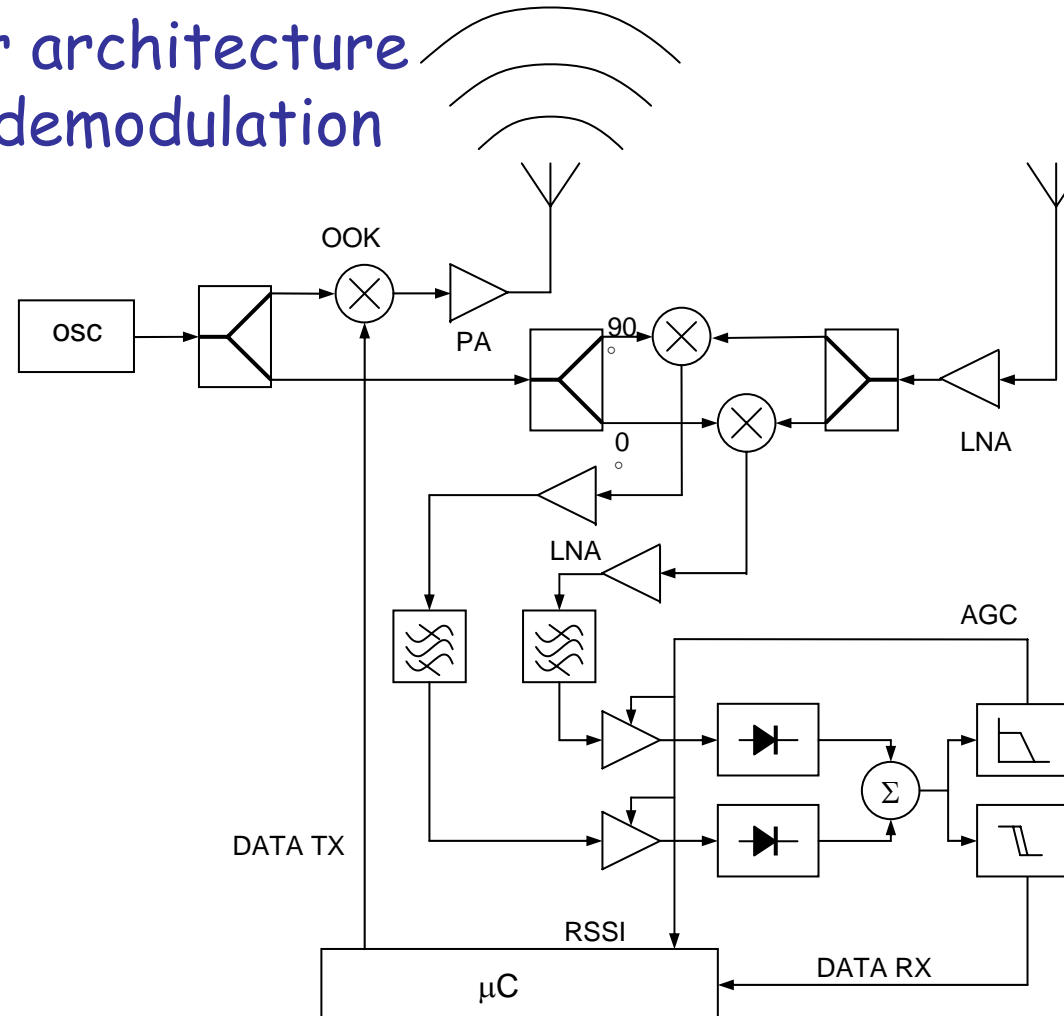Advanced Reader architecture with quadrature demodulation



4 Tag & Reader Design

a Tag Integrated Circuit Design

b Reader Design

Operational Principle


RF Processing

IF Processing



Advanced Reader architecture

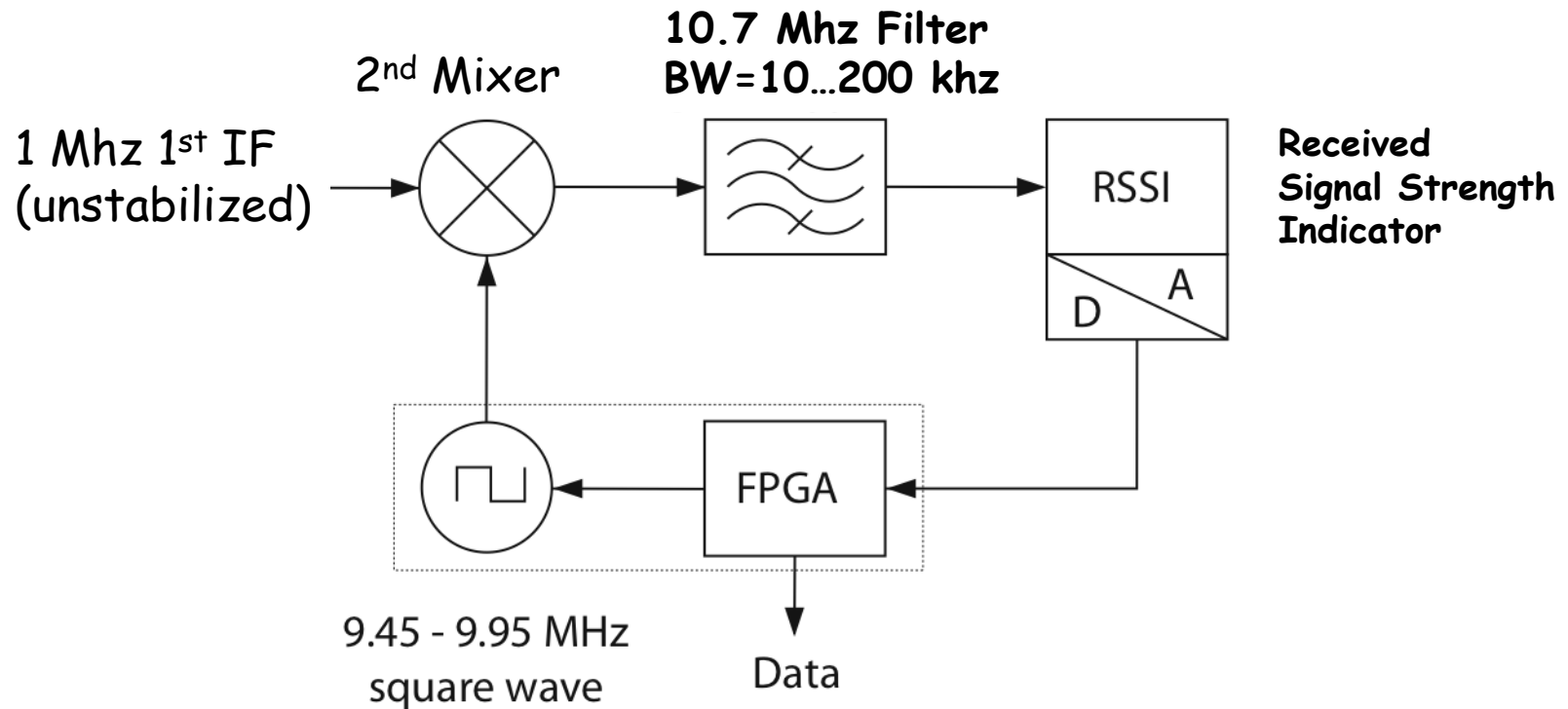2nd IF : Up-conversion with Frequency Sweeping Loop



5

Conclusions

Conclusions



5. CONCLUSION

Conclusions

- Wireless power transmission & rectifier models have been developed for optimizing the power supply available for the tag
- Different backscattering modulation types were compared and pPSK was identified as an excellent candidate given the naturally high input impedance of the tag;
- Readers' main issues were studied and optimized to achieve a sensitivity of -105 dBm @ BER = 10^{-5} & BW = 200 kHz
- Power management of tag circuits and signal encoding has been carefully studied and proved to be a major issue in the overall performance
- A 2.45 GHz tag IC connected to a folded dipole antenna and inductively matched led to a measured reading distance of 12 m;

Acknowledgements



The material presented in this workshop on « Passive UHF RFID Systems » is the result of a team work.

Co-authors are gratefully acknowledged:

Dr. Jari-Pascal Curty
Dr. Catherine Dehollain
Dr. Norbert Joehl

For a detailed information on this topic, please refer to the book « Design and Optimization of Passive UHF RFID Systems » by the same authors, published by Springer (Sept. 2006)